

# Diode Application



1

**EEE 1221**  
**ELECTRONICS**
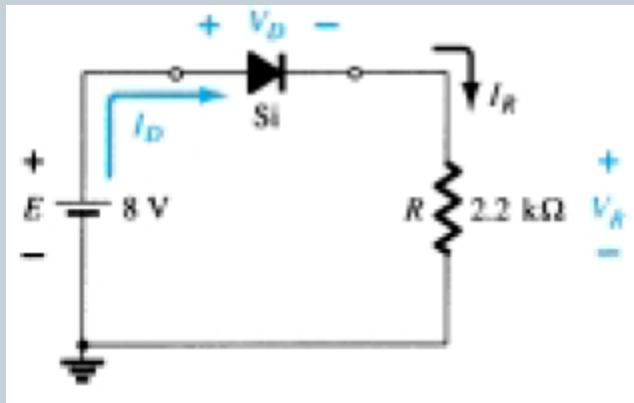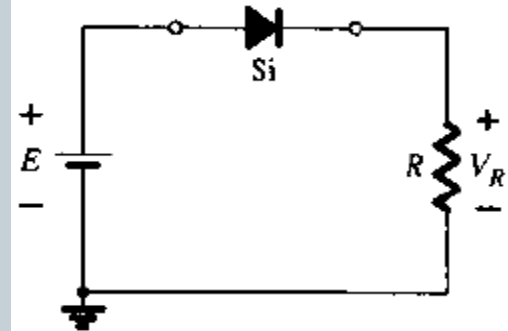
# Series Diode Configuration with DC Inputs

2

$$\begin{aligned}V_D &= V_T \\V_R &= E - V_T \\V_R &= I_D R = I_R R\end{aligned}$$




$$V_D = 0.7\text{ V}$$

$$V_R = E - V_D = 8\text{ V} - 0.7\text{ V} = 7.3\text{ V}$$

$$I_D = I_R = \frac{V_R}{R} = \frac{7.3\text{ V}}{2.2\text{ k}\Omega} \cong 3.32\text{ mA}$$

# Parallel Diode Configuration with DC Inputs


3

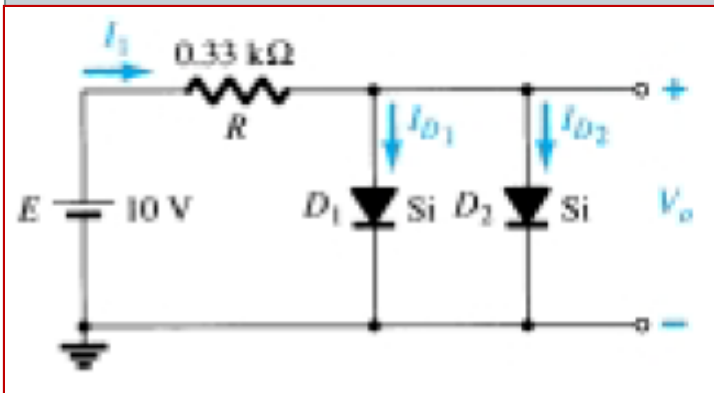

$$I_1 = \frac{V_R}{R} = \frac{E - V_D}{R} = \frac{10 \text{ V} - 0.7 \text{ V}}{0.33 \text{ k}\Omega} = 28.18 \text{ mA}$$

$$I_{D1} = I_{D2} = \frac{I_1}{2} = \frac{28.18 \text{ mA}}{2} = 14.09 \text{ mA}$$


Which Diode will turn on?

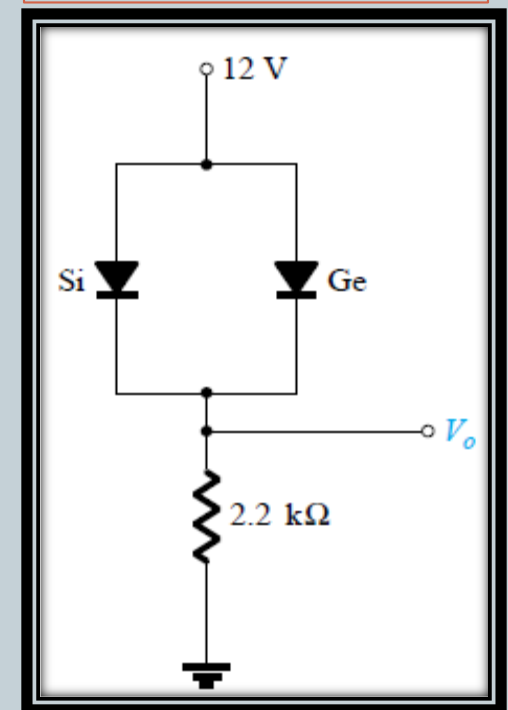

# Series- Parallel Configuration

4

Find the Value of currents.....

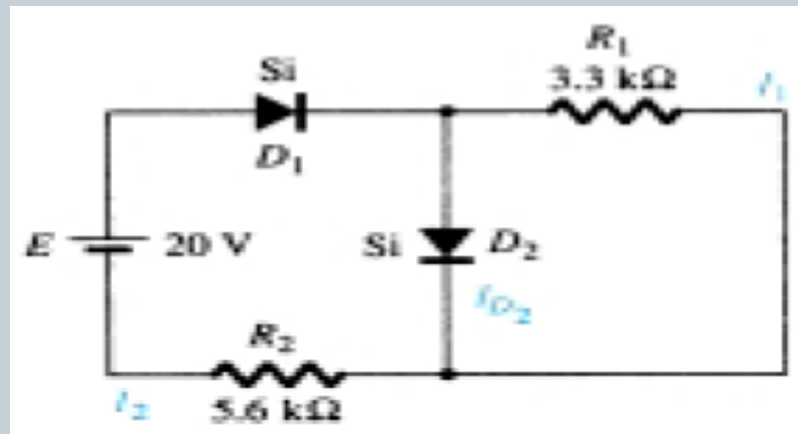

# RECTIFIER

5

❖ An electronic device which converts the ac input voltage to a pulsating dc voltage.

Two types

→ Half wave rectifier

→ Full wave rectifier

# HALF WAVE RECTIFIER

6


- The process of removing one-half the input signal to establish a dc level is called *half-wave rectification*.
- During the positive half cycles diode turns into “on” state because of forward bias and conduct currents.
- During the negative half cycles diode turns into “off” state because of reverse bias so no current flows in that cycles.

# HALF WAVE RECTIFIER

7

## ❖ Positive half cycle


Half Wave Rectifier

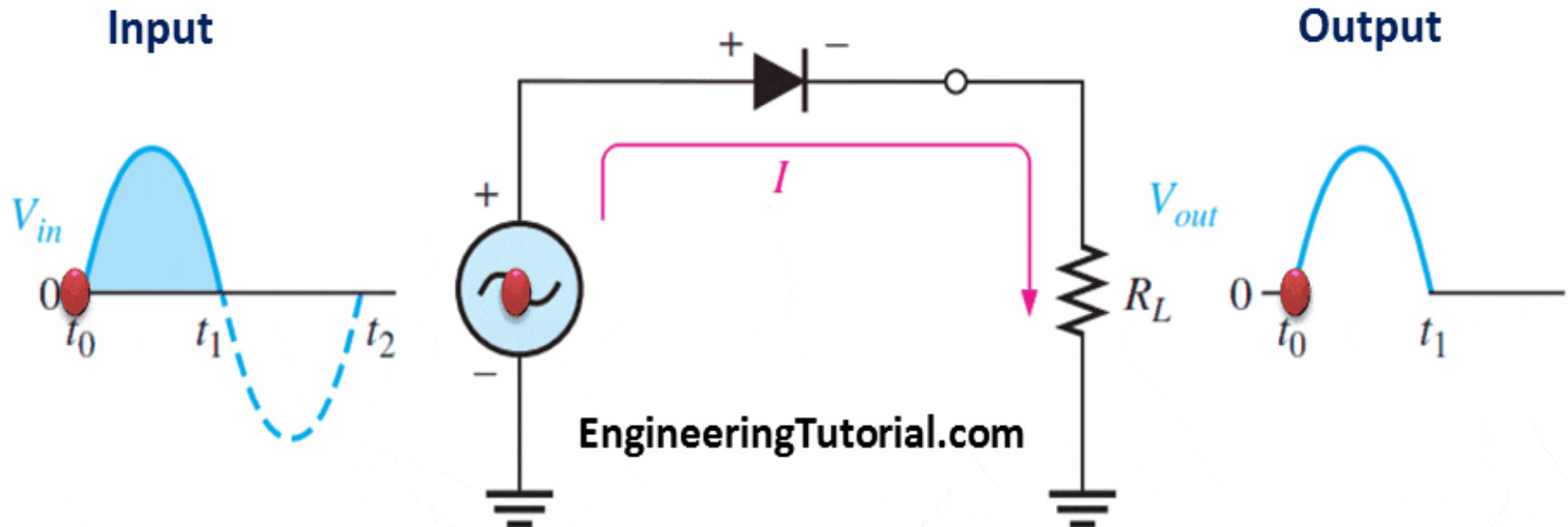

# HALF WAVE RECTIFIER

8

## ❖ Negative half cycle

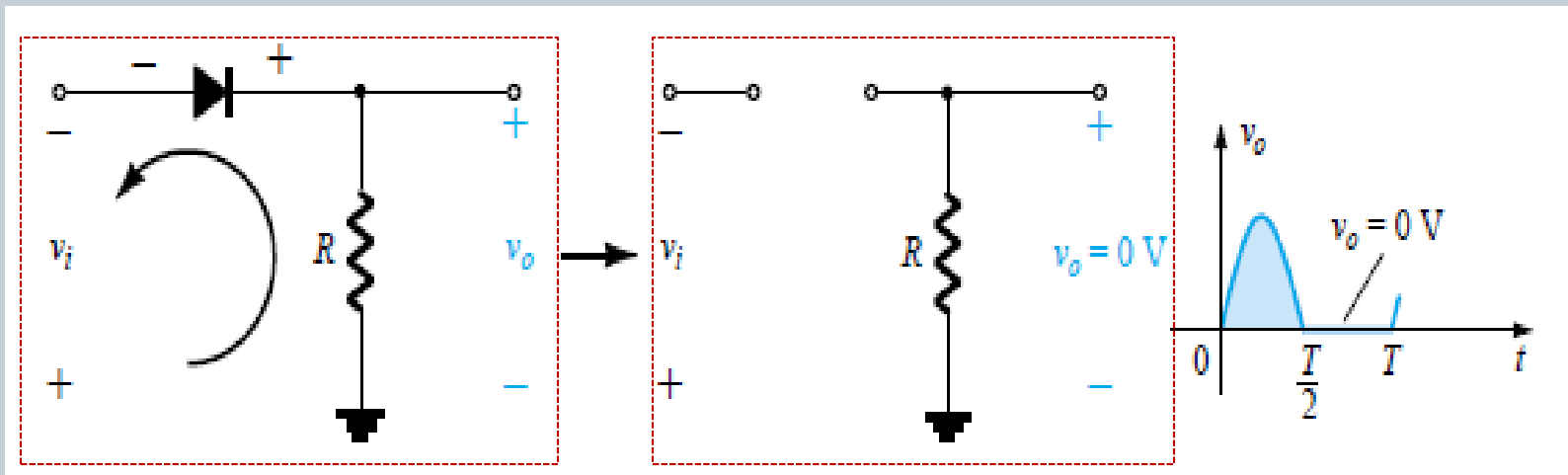




# HALF WAVE RECTIFIER

9

## □ Input Output Waveform:

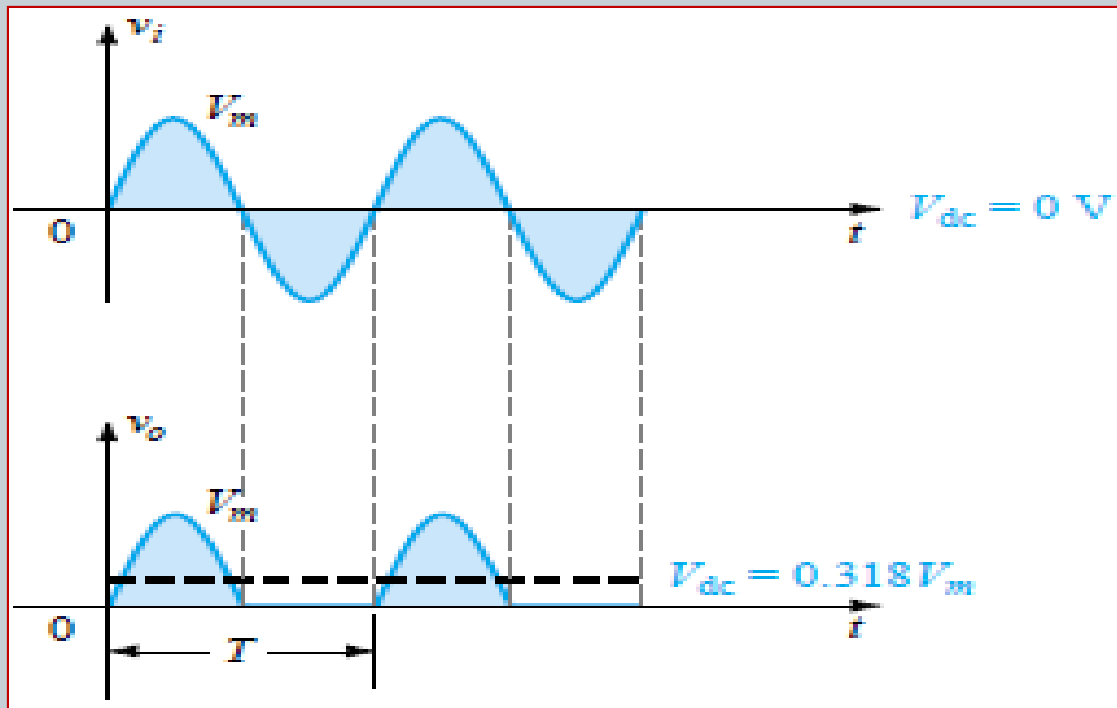


$$V_o = V_{in} = V_m$$

$$V_{avg} = V_{dc} = .318V_m$$

# HALF WAVE RECTIFIER

10

- Effect of Barrier Potential:

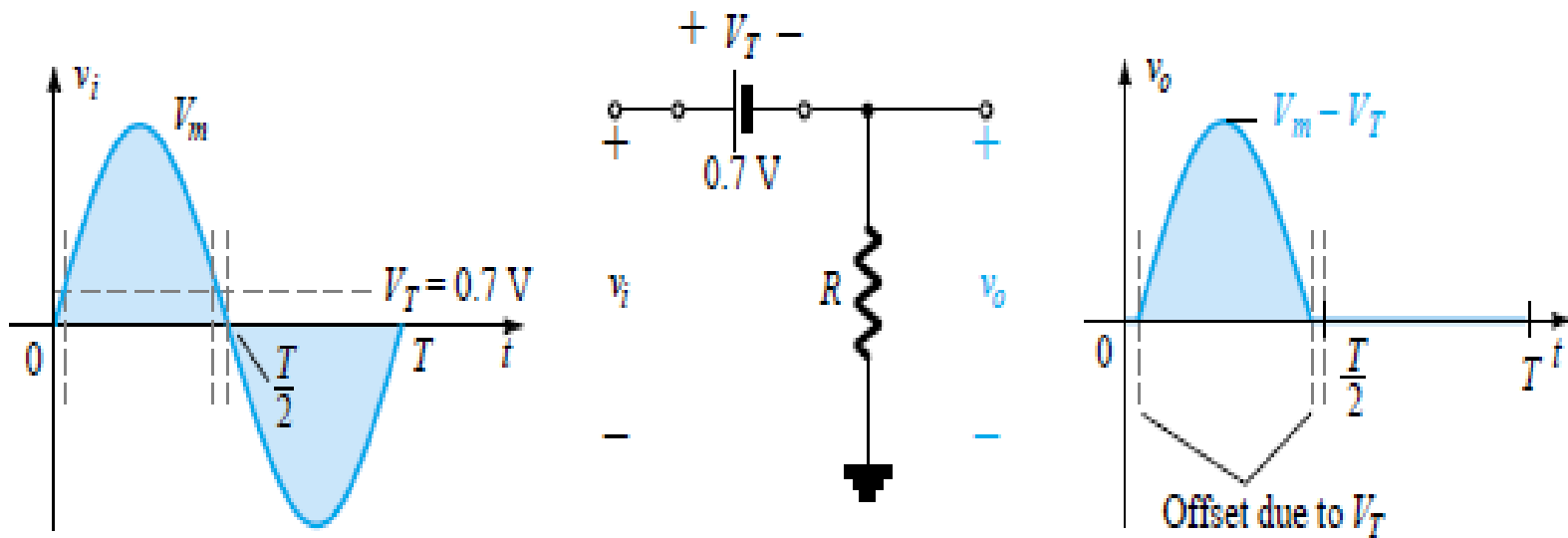

$$V_{avg} = V_{dc} = 0.318 (V_m - V_T)$$

# HALF WAVE RECTIFIER


11

- **Peak Inverse Voltage**

Applying Kirchhoff's voltage law

$$\begin{aligned} V_m &= V(\text{PIV}) + V_o \\ \text{or, } V_m - V_o &= V(\text{PIV}) \end{aligned}$$

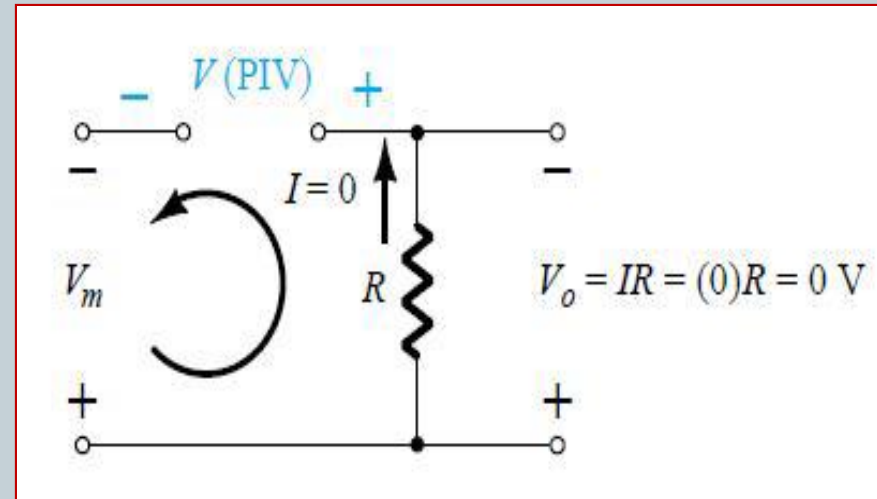
$$\text{PIV rating} \geq V_m \quad \text{half-wave rectifier}$$



# Math Problem

12

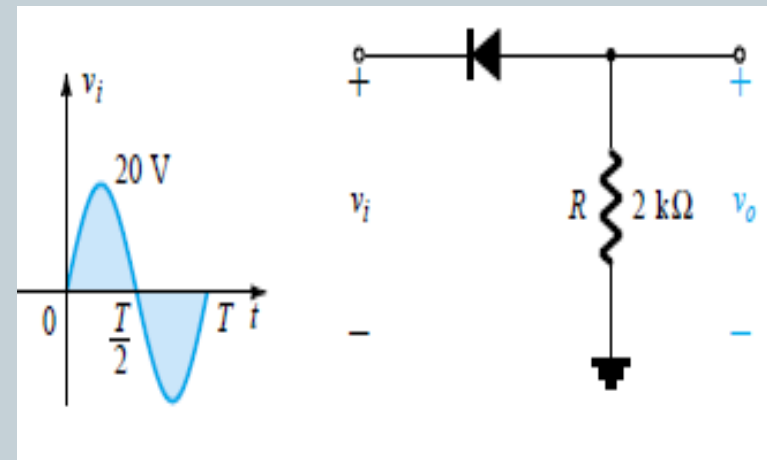
- (a) Sketch the output  $V_o$  and determine the dc level of the output for the network in Fig.
- (b) Repeat part (a) if the ideal diode is replaced by a silicon diode.
- (c) Repeat parts (a) and (b) if  $V_m$  is increased to 200 V and compare solutions.


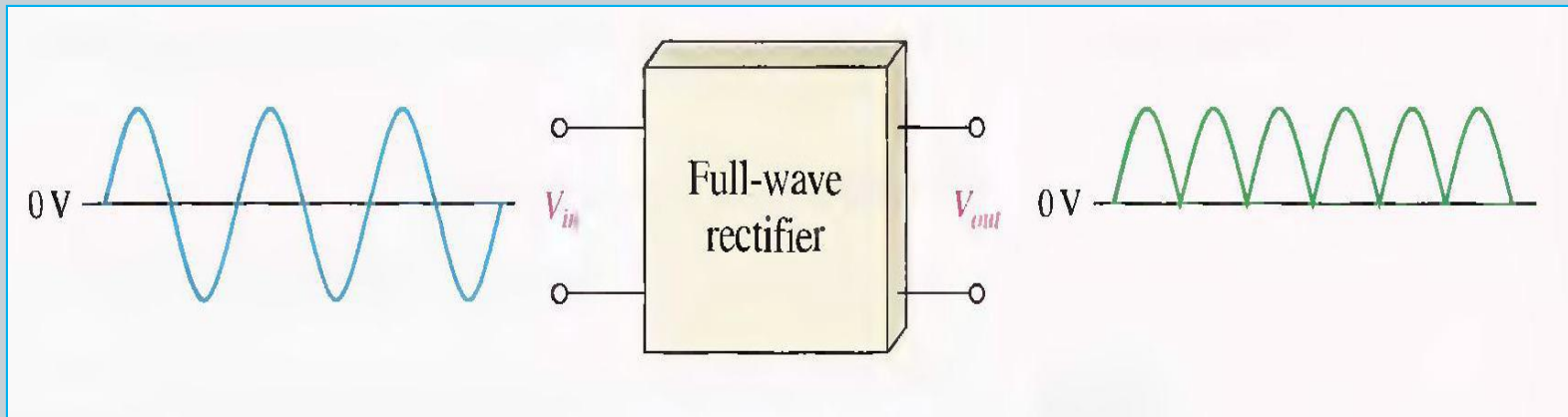
# FULL WAVE RECTIFIER

13

■ The dc level obtained from a sinusoidal input can be improved 100% using a process called ***full-wave rectification***.




- Bridge Full Wave Rectifier
- Center Tapped Full Wave Rectifier

# Bridge Network

14

## ➤ Positive half cycle

### Bridge Full Wave Rectifier

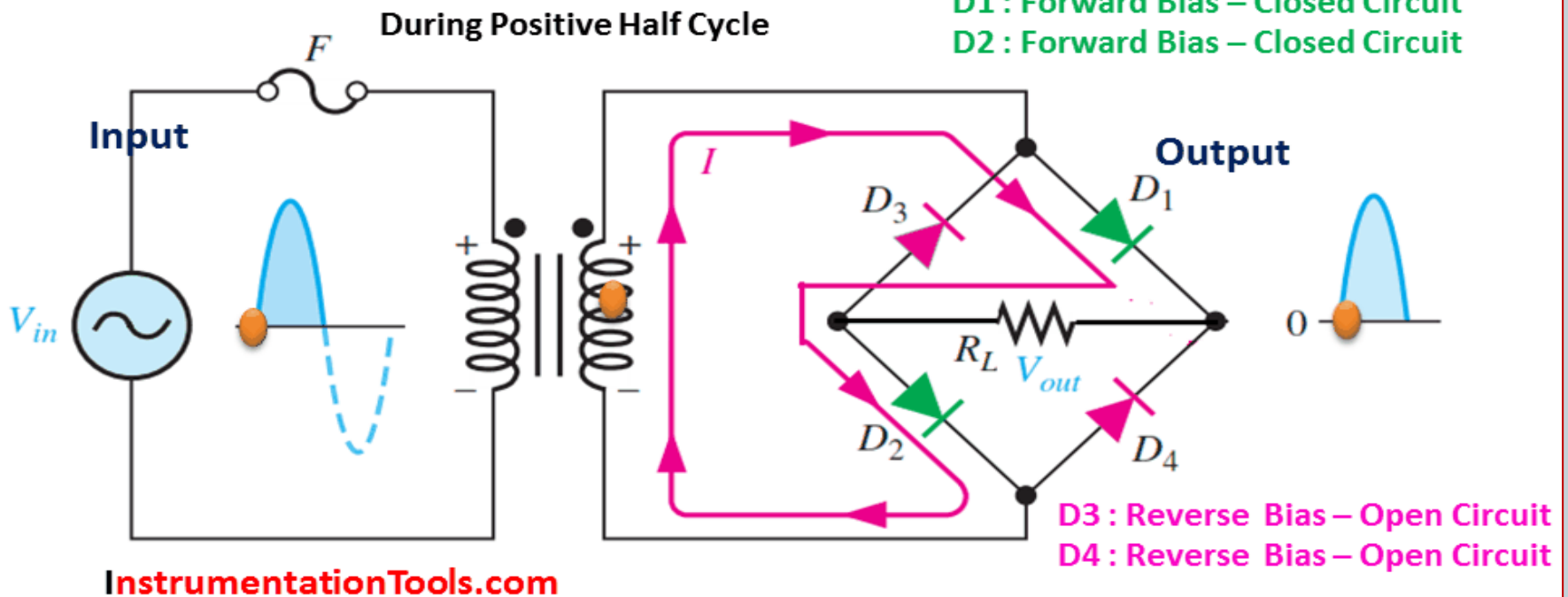


# Bridge Network

15

## ➤ Negative half cycle


### Bridge Full Wave Rectifier

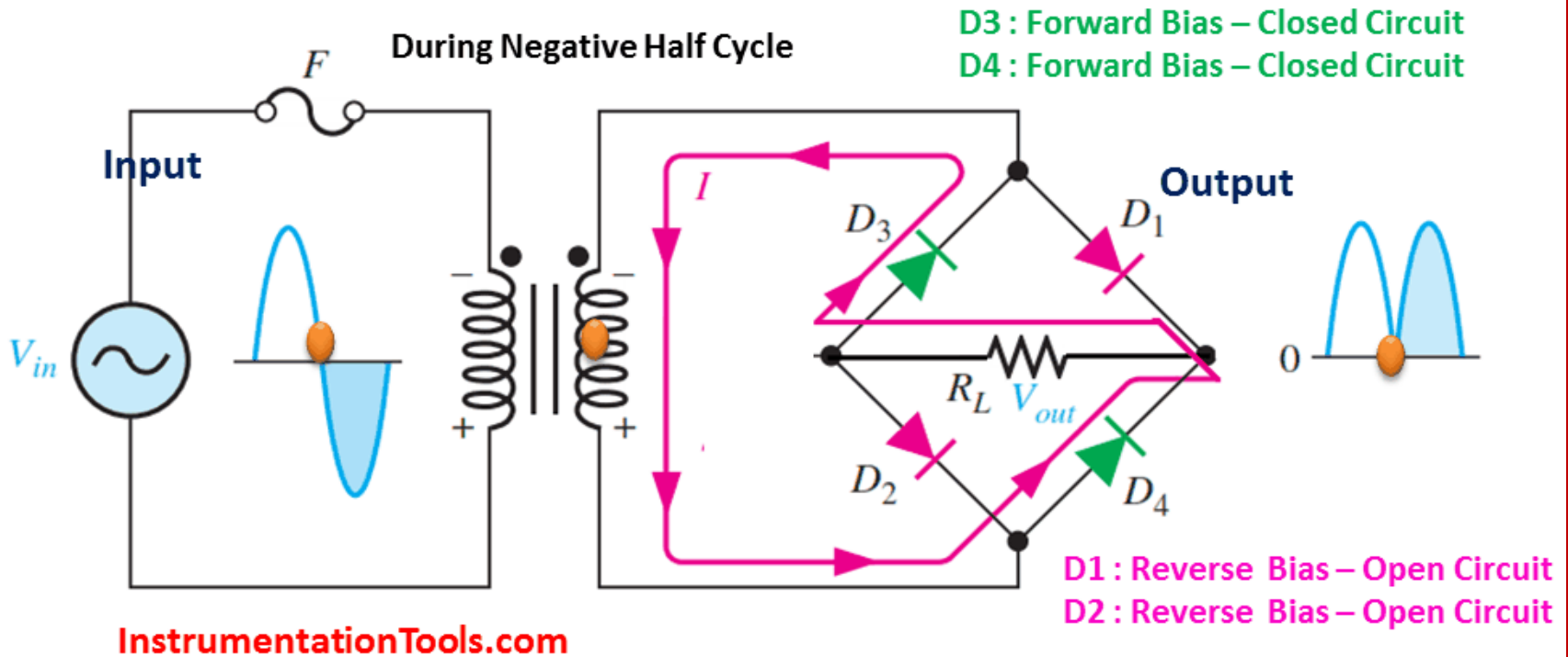

# Bridge Network

16

## Input Output Waveform:

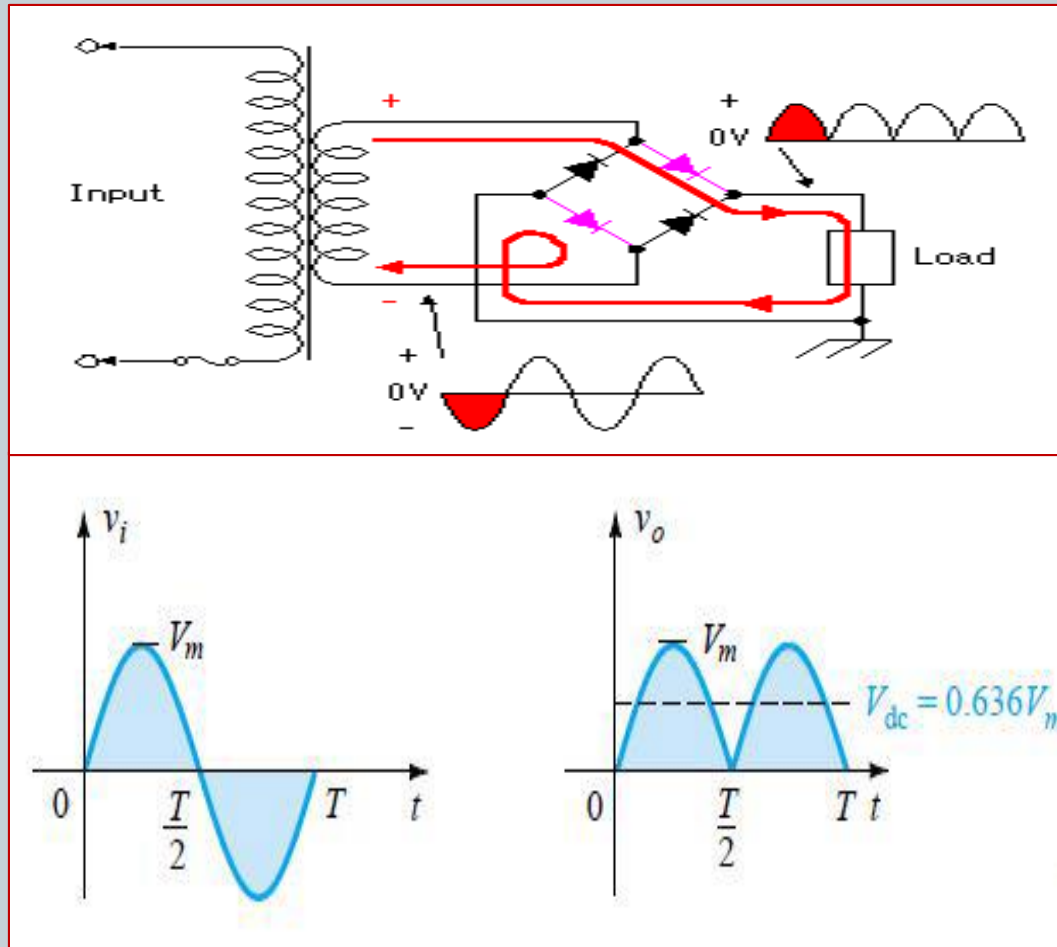

$$V_{out} = V_{in}$$


$$V_{avg} = V_{dc} = 0.636 V_o$$



# Bridge Network

17

- Effect of Barrier Potential:

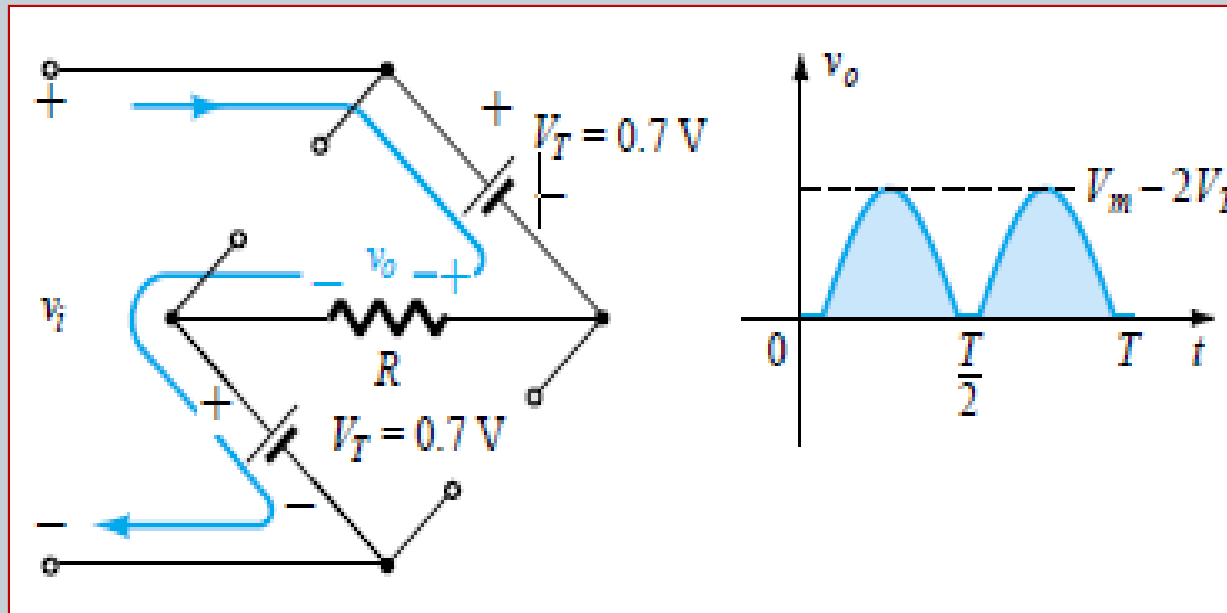


$$V_{avg} = V_{dc} = 0.636 (V_m - 2V_T)$$

# Bridge Network

18

- Peak Inverse Voltage:
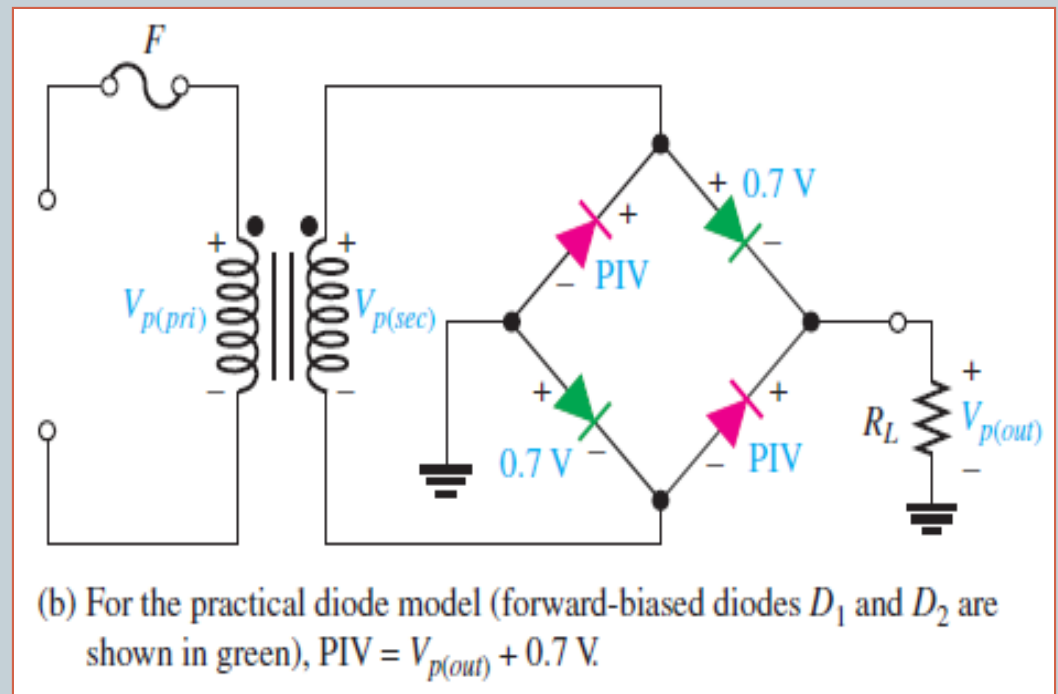
$$\begin{aligned} \text{PIV} &= V_p(\text{out}) + V_T \\ &= V_m + V_T \end{aligned}$$



# Math Problem

19

Determine the peak output voltage for the bridge rectifier in Figure 2–41. Assuming the practical model, what PIV rating is required for the diodes? The transformer is specified to have a 12 V rms secondary voltage for the standard 120 V across the primary.


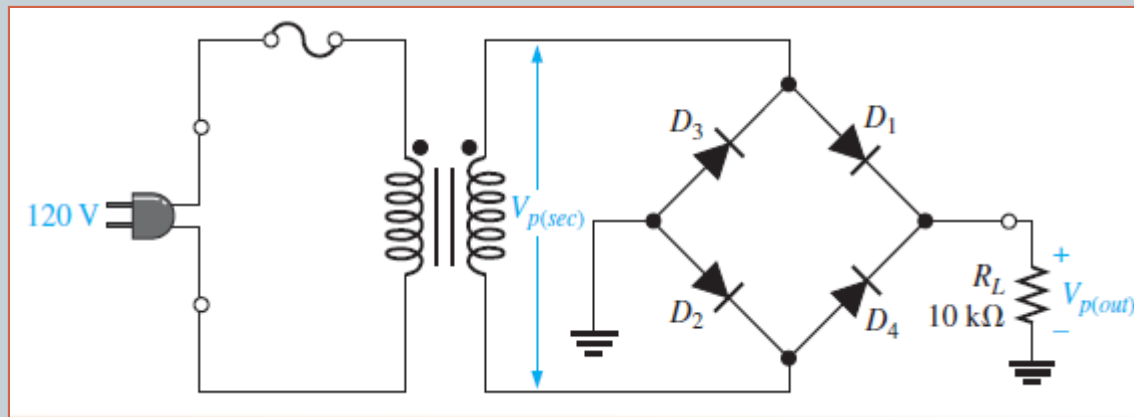


FIGURE 2–41
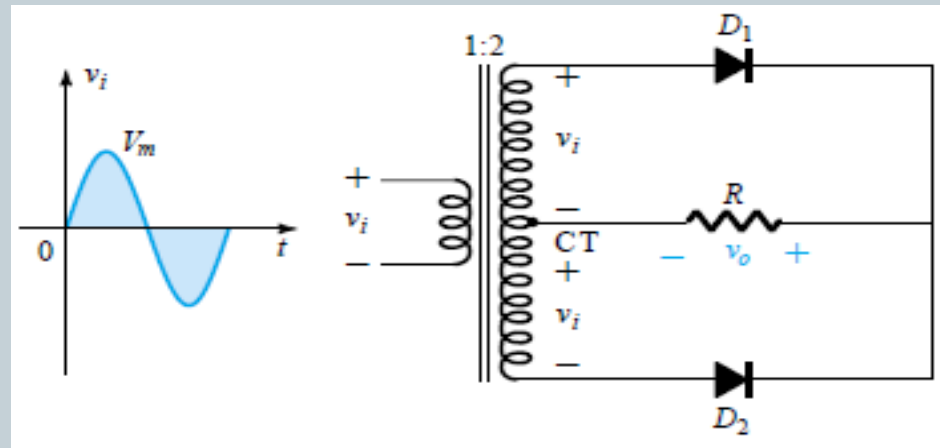
# Center Tapped Full Wave Rectifier

20

- A second popular full-wave rectifier appears in Fig. with only two diodes but requiring a center-tapped (CT) transformer to establish the input signal across each section of the secondary of the transformer.



# Center Tapped Full Wave Rectifier


21

## ➤ Positive half cycle

### Center Tapped Full Wave Rectifier

During Positive Half Cycle

$D_1$  : Forward Bias – Closed Circuit

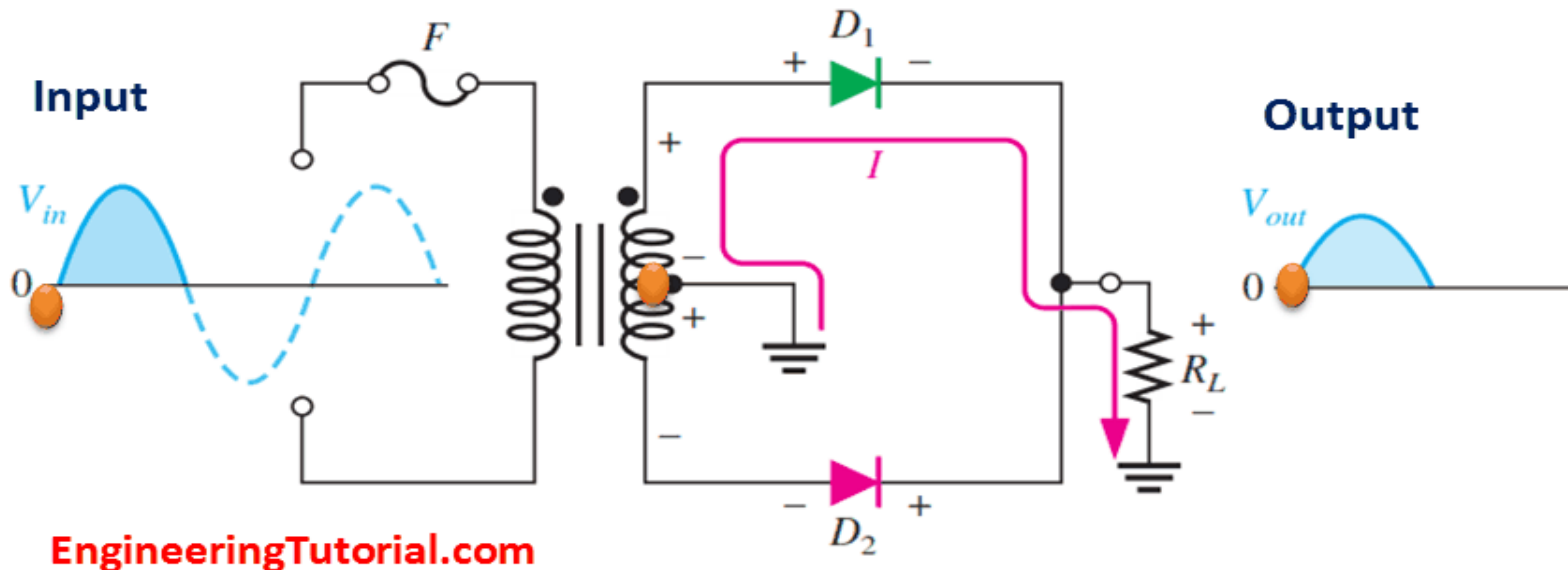


$D_2$  : Reverse Bias – Open Circuit

# Center Tapped Full Wave Rectifier

22

## ➤ Negative half cycle


### Center Tapped Full Wave Rectifier

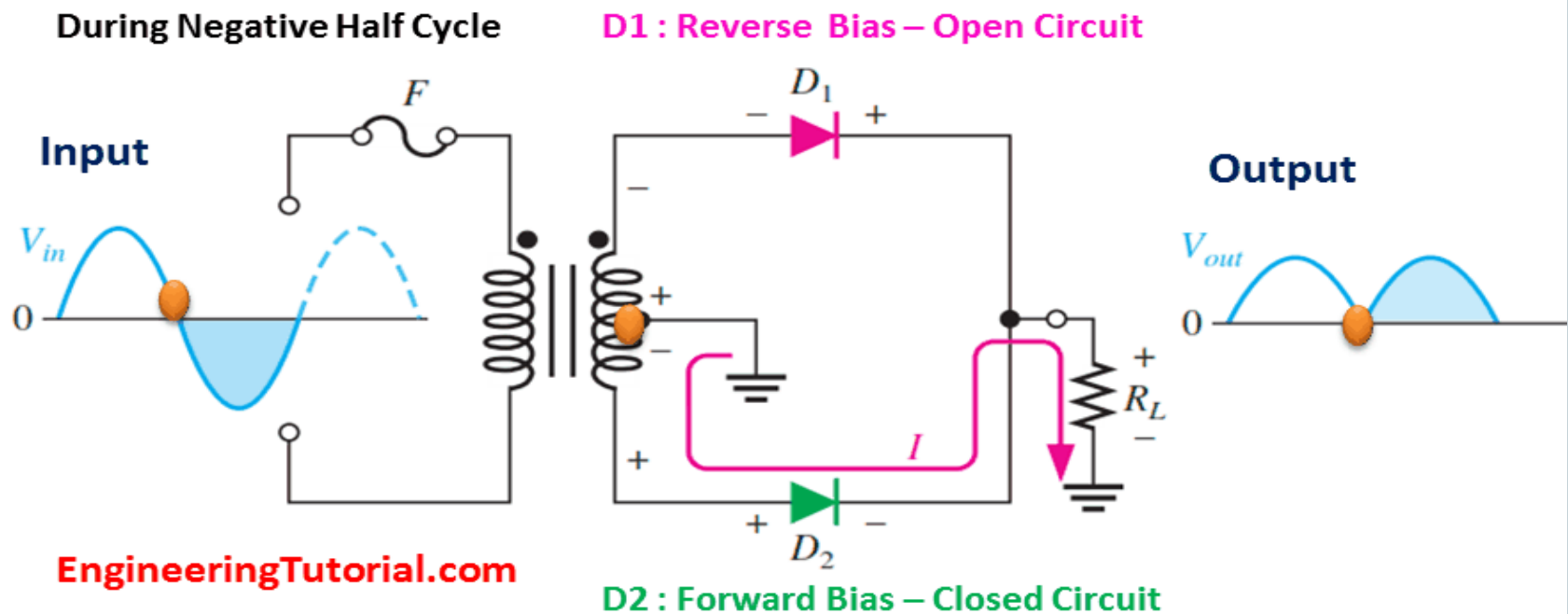

# Center Tapped Full Wave Rectifier

23

- **Input- Output Waveform:**

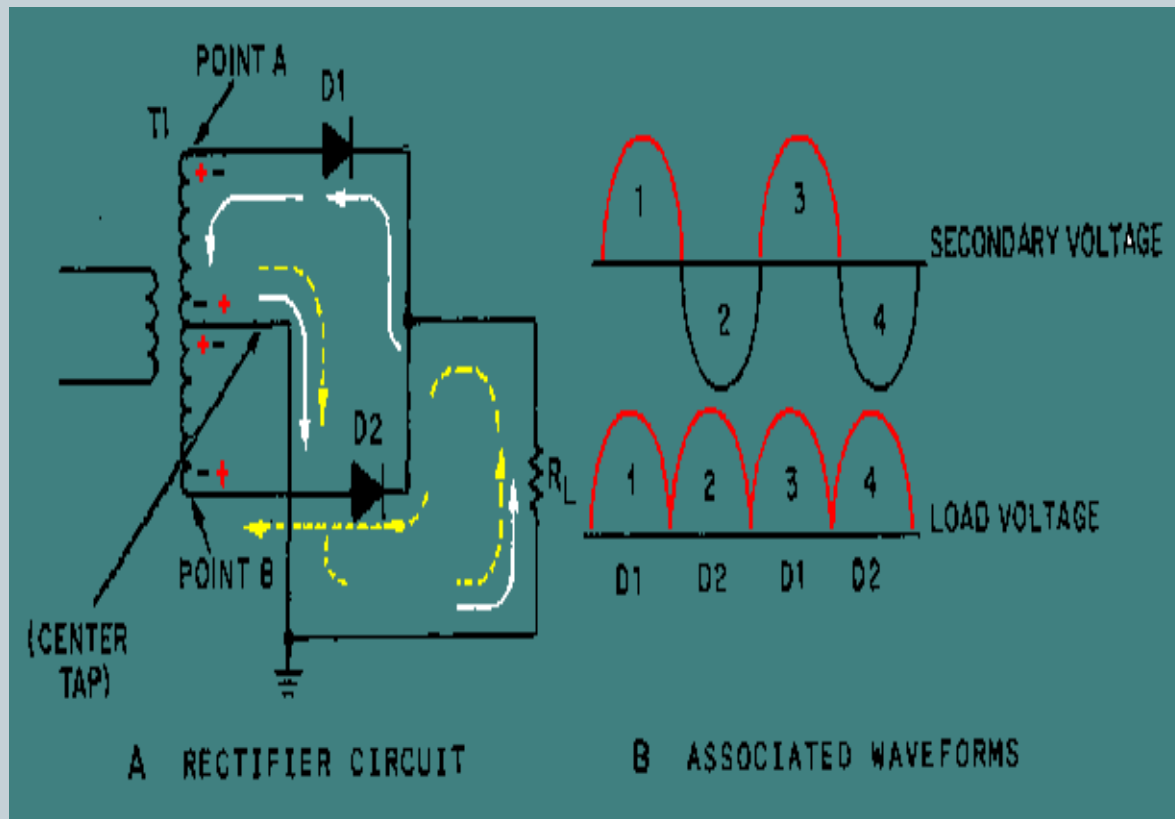

Turn Ratio  
(1:2)


$$V_o = V_{\text{sec}} / 2$$

$$V_{\text{avg}} = V_{\text{dc}} \\ = 0.636 V_o$$

# Center Tapped Full Wave Rectifier

24

- Peak Inverse Voltage

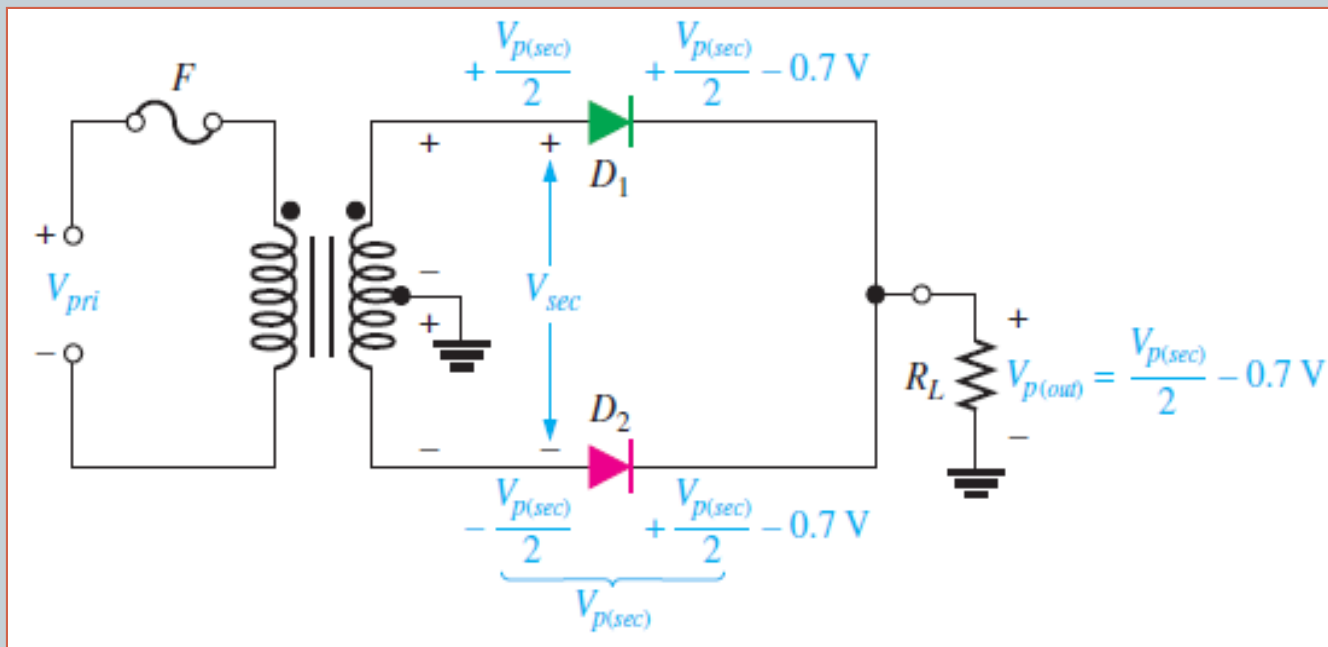


$$PIV = V_{sec} - V_T$$



# Math Problem

25

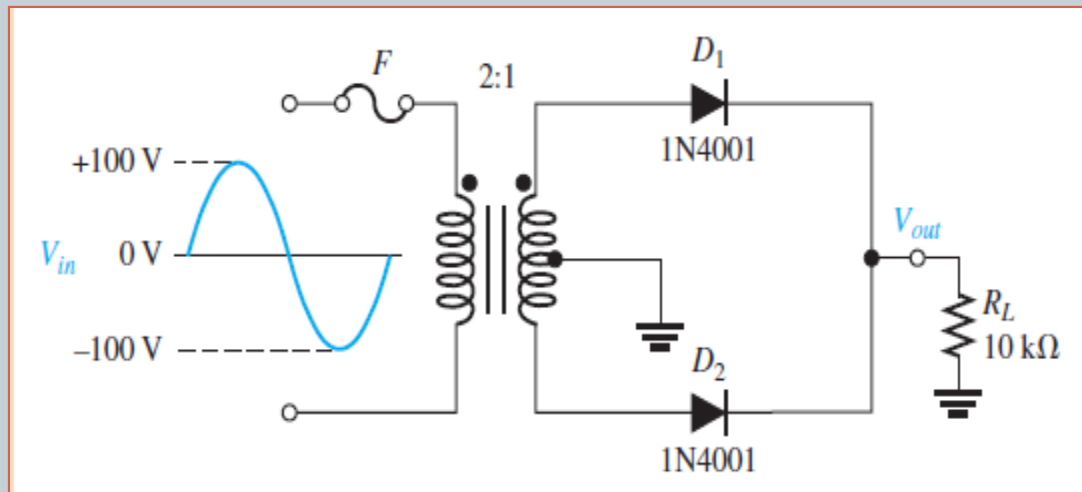- (a) Show the voltage waveforms across each half of the secondary winding and across  $R_L$  when a 100 V peak sine wave is applied to the primary winding in Figure 2–36.
- (b) What minimum PIV rating must the diodes have?



# WHICH ONE IS BETTER?


26

- Center tap rectification?
- Bridge rectification?
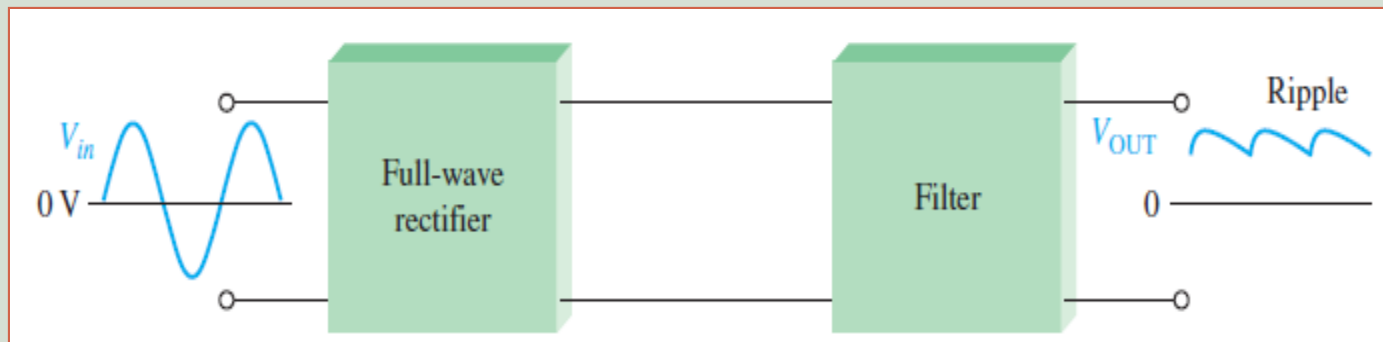
# Filter


27

- A power supply filter ideally eliminates the fluctuations in the output voltage of half wave or full-wave rectifier and produces a constant-level dc voltage.



# Capacitor Input Filter


28

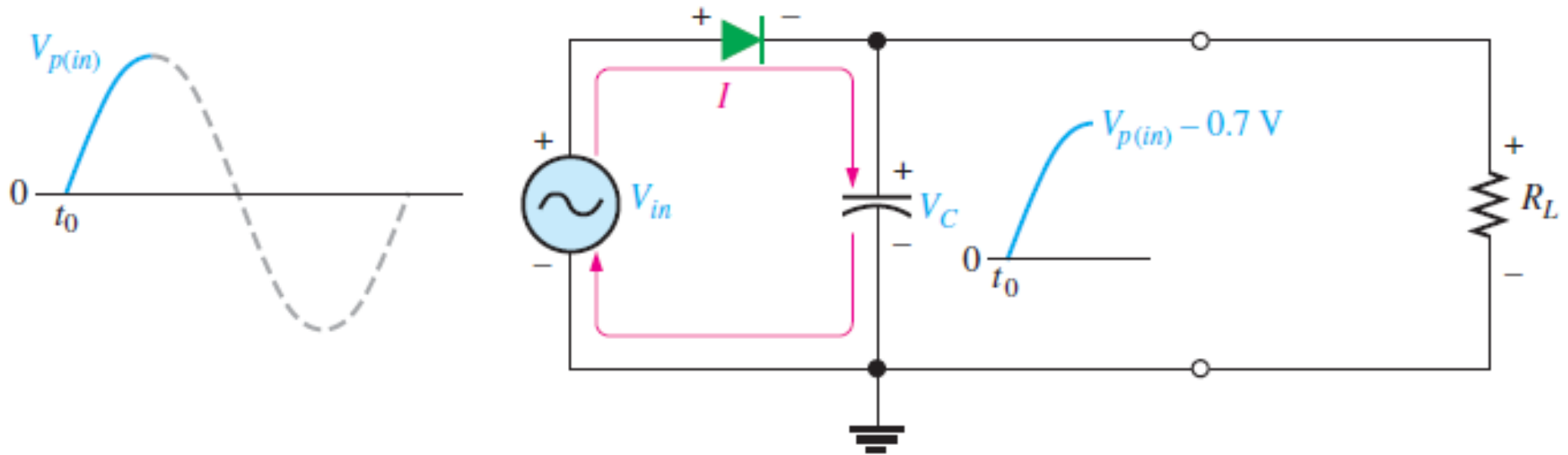

(a) Initial charging of the capacitor (diode is forward-biased) happens only once when power is turned on.

# Capacitor Input Filter


29

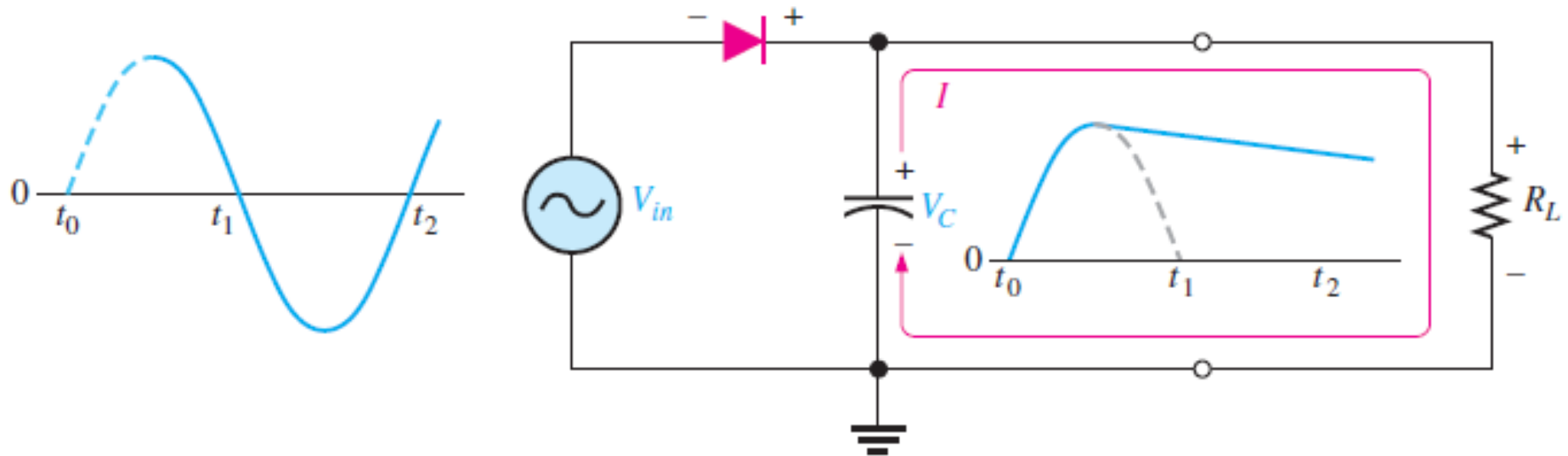

- (b) The capacitor discharges through  $R_L$  after peak of positive alternation when the diode is reverse-biased. This discharging occurs during the portion of the input voltage indicated by the solid dark blue curve.




# Capacitor Input Filter

30

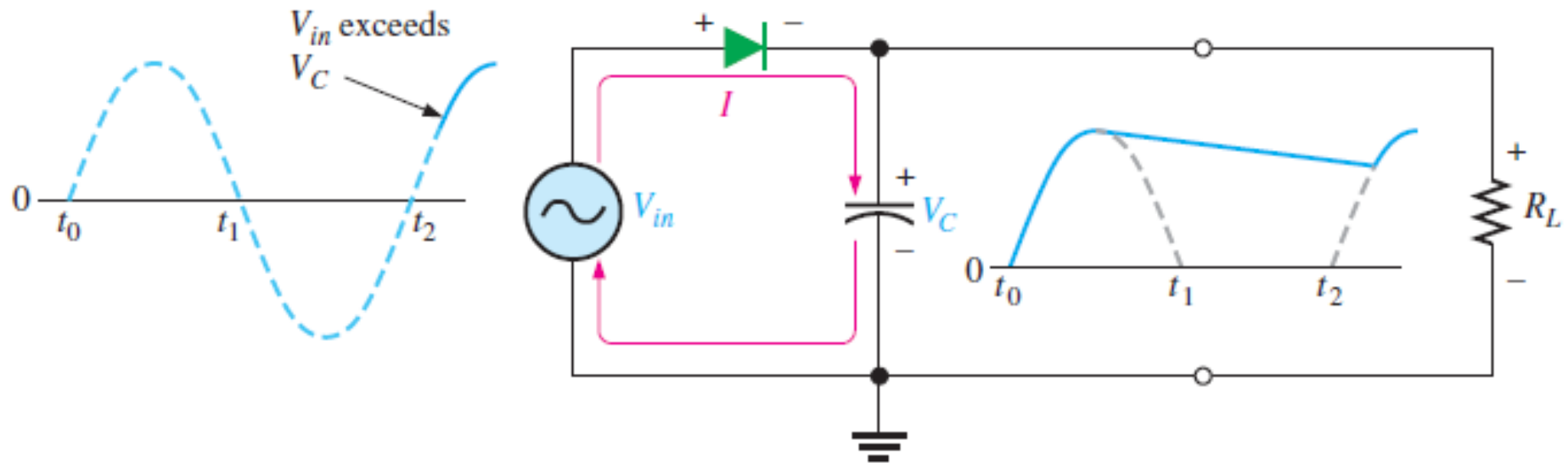

(c) The capacitor charges back to peak of input when the diode becomes forward-biased. This charging occurs during the portion of the input voltage indicated by the solid dark blue curve.

# Capacitor Input Filter

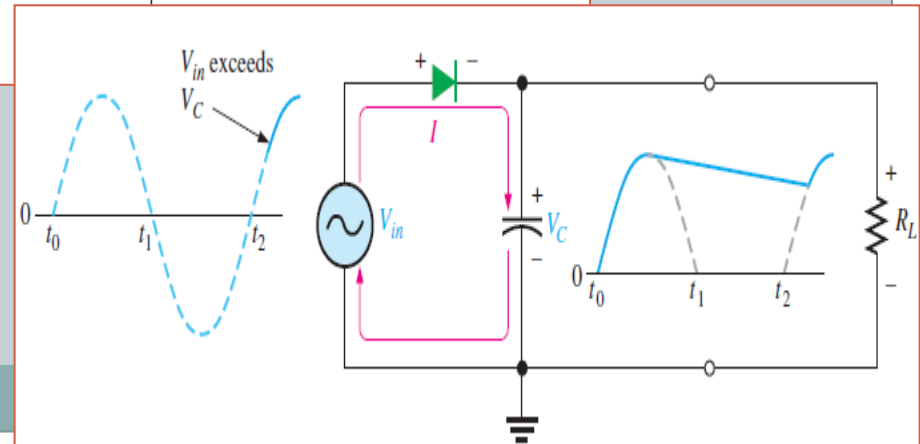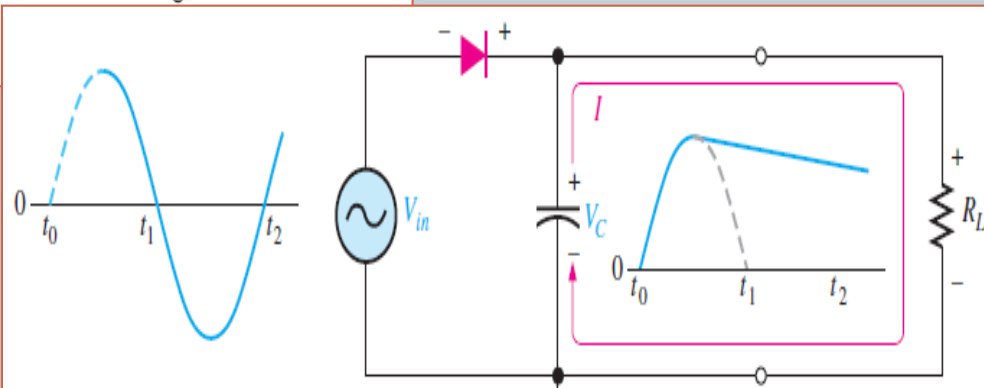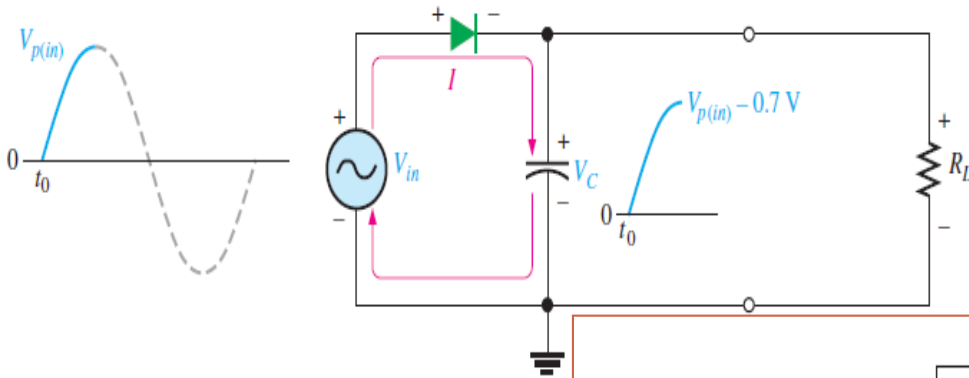

# Ripple Voltage



32

- The variation in the capacitor voltage due to the charging and discharging is called the **ripple voltage**.
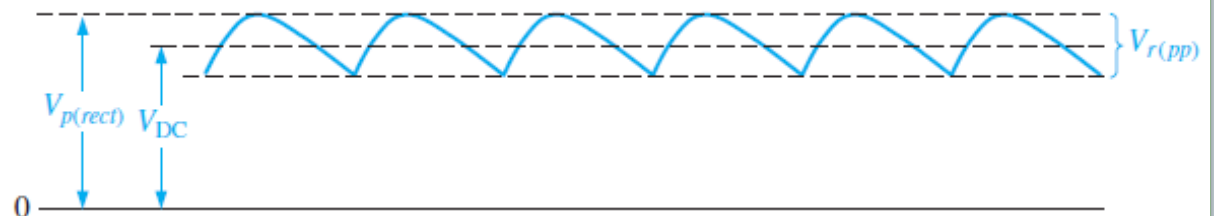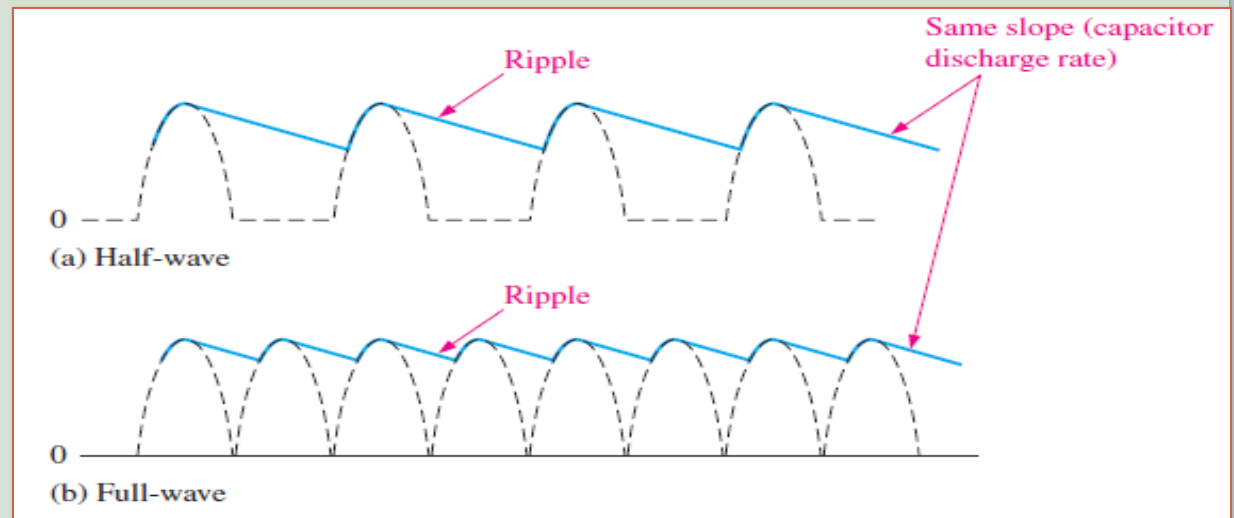
## Ripple Factor

$$r = \frac{V_{r(pp)}}{V_{DC}}$$


$$V_{r(pp)} \cong \left( \frac{1}{fR_L C} \right) V_{p(rect)}$$
$$V_{DC} \cong \left( 1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$




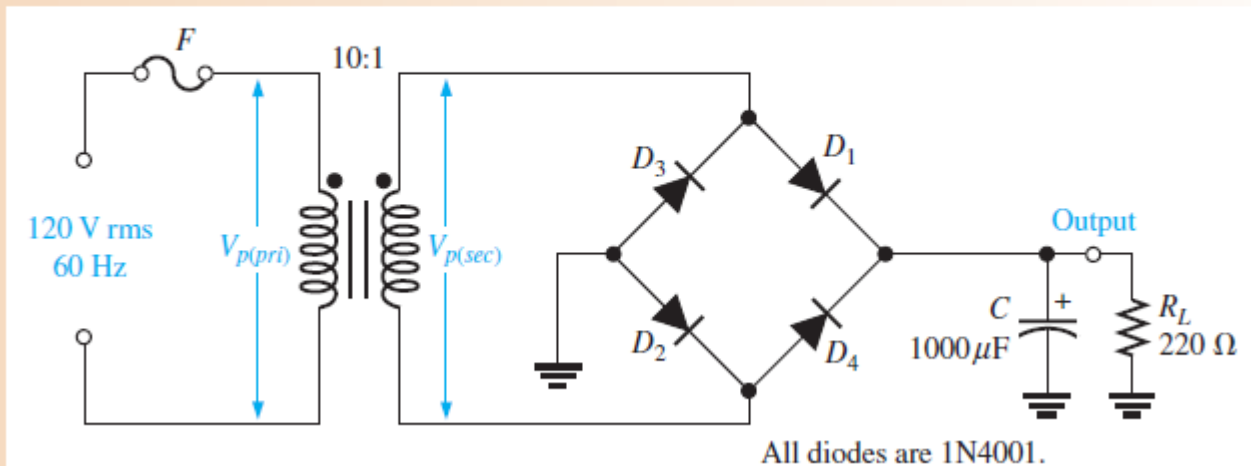
# Math Problem

Determine the ripple factor for the filtered bridge rectifier with a load as indicated in Figure 2-48.



$$r = \frac{V_{r(pp)}}{V_{DC}}$$

$$V_{r(pp)} \cong \left( \frac{1}{fR_L C} \right) V_{p(rect)}$$

$$V_{DC} \cong \left( 1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$

$$V_{r(pp)} \cong \left( \frac{1}{fR_L C} \right) V_{p(rect)} = \left( \frac{1}{(120 \text{ Hz})(220 \Omega)(1000 \mu\text{F})} \right) 15.6 \text{ V} = 0.591 \text{ V}$$

$$V_{DC} = \left( 1 - \frac{1}{2fR_L C} \right) V_{p(rect)} = \left( 1 - \frac{1}{(240 \text{ Hz})(220 \Omega)(1000 \mu\text{F})} \right) 15.6 \text{ V} = 15.3 \text{ V}$$

$$r = \frac{V_{r(pp)}}{V_{DC}} = \frac{0.591 \text{ V}}{15.3 \text{ V}} = \mathbf{0.039}$$

# Self Topic

34

- Surge Current in the Capacitor Input Voltage
- Voltage Regulators

# SELF-STUDY

35

**Do All Mathematics Problem Of  
Example And Exercise From The  
Reference Book !!!!**

# Reference

36

- Half wave & Full wave
- <https://electronicscoach.com/difference-between-centre-tapped-and-bridge-rectifier.html>
- <https://www.elprocus.com/full-wave-bridge-rectifier-versus-center-tapped-full-wave-rectifier/>

THANK YOU!!!

*ANY QUESTION ?*