

International Islamic University Chittagong

Department of Electrical and Electronic Engineering

Final Examination Spring-2018

Course Code: EEE 1101

Time: 2 hours 30 minutes

Program: B.Sc. Engg. (EEE)

Course Title: Electrical Circuit-I

Full Marks: 50

Part A

[Answer any two questions from the followings; figures in the right margin indicate full marks.]

- 1(a). Use source conversion technique to find the load current in the following circuit in Fig.1a, for the resistor between point A-B. Consider the values of all registers in the circuit in ohm. 05

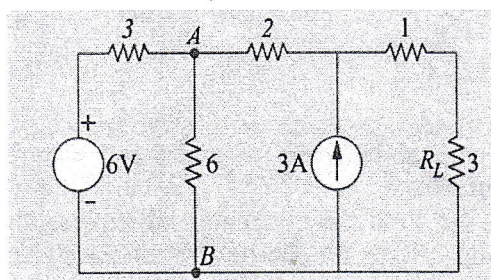


Fig.1a

- 1(b). Use superposition theorem to find the current I in the following circuit in Fig.1b. Consider the values of all registers in the circuit in ohm. 05

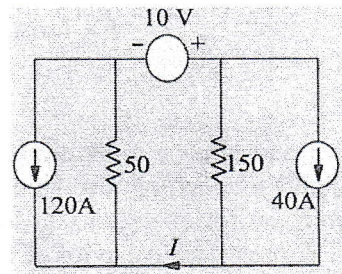


Fig.1b

- 2(a). State and explain maximum power transfer theorem. Deduce the condition for the maximum power. 04

- 2(b). Calculate the value of R in Fig.2 to be maximum power to load R . 06

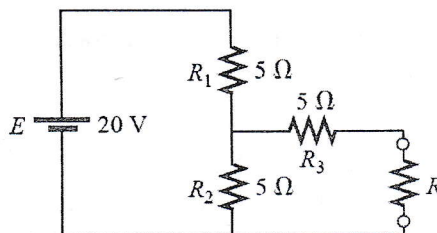


Fig.2

- 3(a). Find V_{th} and R_{th} between the terminals a-b of the circuit in Fig.3a. 05

- 3(b). Determine the Norton equivalent network from the given network in Fig.3b. 05

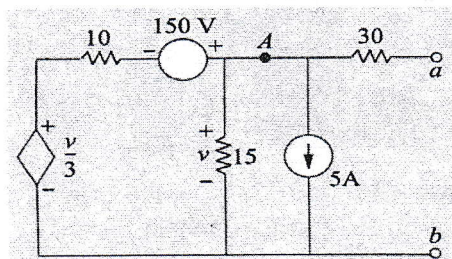


Fig.3a

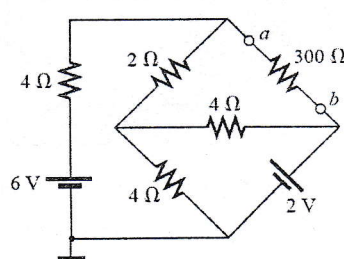


Fig.3b.

Part B

[Answer any three questions from the followings]

- 4(a). Three capacitors C_1 , C_2 and C_3 are connected in parallel and the corresponding equivalent capacitance is C_p . Derive the equation for C_p . 04
- 4(b). Describe the transient behaviors of series R-C circuit for charging and discharging phases with necessary equations, circuit diagrams and curves. 06
- 5(a). Define permeability, magnetizing force, hysteresis and flux density. 04
- 5(b). Find the magnetic flux ϕ for the series magnetic circuit in Fig.4 for the specified impressed mmf. 06

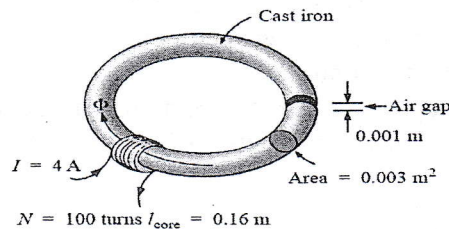


Fig.4

- 6(a). Describe ampere's circuital law. Compare between magnetic and electric circuits mentioning the analogous variables. 05
- 6(b). From the following circuit in Fig.5. (i). Find the mathematical expressions for the transient behavior of V_C , i_C , and V_R for the circuit of when the switch is moved to position 1. Plot the curves of V_C , i_C , and V_R . (ii). How much time must pass before it can be assumed, for all practical purposes, that $i_C = 0$ A and $V_C = E$ volts? 05


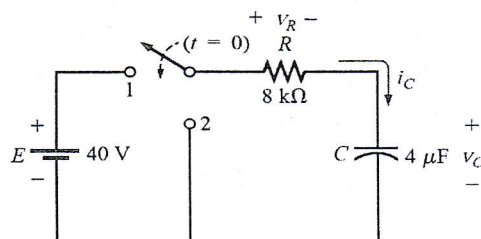


Fig.5

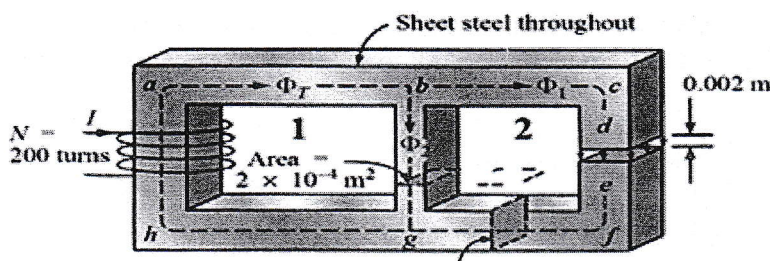- 7(a). Derive the expression of energy stored in an inductor. 05
- 7(b). For the series-parallel magnetic circuit in Fig.6, find the value of I required to establish a flux of $\phi_g = 2 \times 10^{-4}$ Wb in the gap. 05



Area for sections other than $bg = 5 \times 10^{-4} \text{ m}^2$
 $l_{ab} = l_{bg} = l_{gh} = l_{ha} = 0.2 \text{ m}$; $l_{bc} = l_{fg} = 0.1 \text{ m}$; $l_{cd} = l_{dg} = 0.099 \text{ m}$

Fig.6