

CSE_2323

Combinational Logic

Digital Logic Design

Course code: CSE-2323

Credit Hour: 3

Md. Mujibur Rahman Maruf

Adjunct Lecturer,


Dept. of CSE, IIUC

Mujiburmaruf.cuet17@gmail.com

International Islamic University Chittagong(IIUC)

Carry look ahead adder

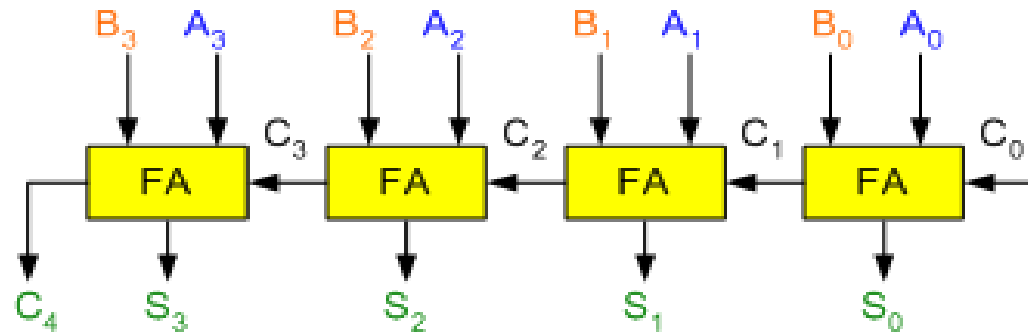
In *ripple carry adders*, the carry propagation time is the major speed limiting factor




carry look-ahead solves carry propagation delay of adders by calculating the carry signals in advance, based on the input signals.

Carry look ahead adder

 let's consider the case of adding two n -bit numbers A and B



 The Figure shows the full adder circuit used to add the operand bits in the i^{th} column; namely A_i & B_i and the carry bit coming from the previous column (C_i).



Carry look ahead adder

In this circuit, the 2 internal signals P_i and G_i are given by:

$$P_i = A_i \oplus B_i \quad (1)$$

$$G_i = A_i B_i \dots \dots \dots (2)$$


The output sum and carry can be defined as :

$$S_i = P_i \oplus C_i \quad (3)$$

$$C_{i+1} = G_i + P_i C_i \quad (4)$$

G_i is known as the **carry Generate** signal since a carry (C_{i+1}) is generated whenever $G_i = 1$, regardless of the input carry (C_i).

 P_i is known as the **carry propagate** signal since whenever $P_i = 1$, the input carry is propagated to the output carry, i.e., $C_{i+1} = C_i$ (note that whenever $P_i = 1$, $G_i = 0$).



Carry look ahead adder

Computed values of *all* the P_i 's are valid one *XOR-gate delay* after the operands A and B are made valid.

Computed values of *all* the G_i 's are valid one *AND-gate delay* after the operands A and B are made valid.

The Boolean expression of the carry outputs of various stages can be written as follows:


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) \\ = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + \\ P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \\ C_4 = G_3 + P_3 C_3 \\ = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

In general, the i^{th} carry output is expressed in the form $C_i = F_i(P's, G's, C_0)$.

 In other words, each carry signal is expressed as a direct SOP function of C_0 rather than its preceding carry signal



Carry look ahead adder


First level: Generates all the P & G signals. Four sets of P & G logic (each consists of an XOR gate and an AND gate). Output signals of this level (P's & G's) will be valid after $1t$.

Second level: The Carry Look-Ahead (CLA) logic block which consists of four 2-level implementation logic circuits. It generates the carry signals (C_1 , C_2 , C_3 , and C_4) as defined by the above expressions. Output signals of this level (C_1 , C_2 , C_3 , and C_4) will be valid after $3t$.

Third level: Four XOR gates which generate the sum signals (S_i) ($S_i = P_i \oplus C_i$). Output signals of this level (S_0 , S_1 , S_2 , and S_3) will be valid after $4t$.

Thus, the 4 Sum signals (S_0 , S_1 , S_2 & S_3) will all be valid after a total delay of $4t$ compared to a delay of $(2n+1)t$ for Ripple Carry adders.

 For a 4-bit adder ($n = 4$), the Ripple Carry adder delay is $9t$.





BCD Adder

Four bits are needed to represent all BCD digits (0 - 9). But with four bits we can represent up to 16 values (0000 through 1111). The extra six values (1010 through 1111) are **not valid** BCD digits

A BCD adder is a circuit that adds two BCD digits in parallel and produces a sum BCD digit and a carry out bit.

  The maximum sum result of a BCD input adder can be 19. As maximum number in BCD is 9 and may be there will be a carry from previous stage also, so $9 + 9 + 1 = 19$



BCD Adder

K	Binary Sum				C	BCD Sum				Decimal
	Z ₈	Z ₄	Z ₂	Z ₁		S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	→ 0	0	0	0	0	0
0	0	0	0	1	→ 0	0	0	0	1	1
0	0	0	1	0	→ 0	0	0	1	0	2
0	0	0	1	1	→ 0	0	0	1	1	3
0	0	1	0	0	→ 0	0	1	0	0	4
0	0	1	0	1	→ 0	0	1	0	1	5
0	0	1	1	0	→ 0	0	1	1	0	6
0	0	1	1	1	→ 0	0	1	1	1	7
0	1	0	0	0	→ 0	1	0	0	0	8
0	1	0	0	1	→ 0	1	0	0	1	9
0	1	0	1	0	→ 1	0	0	0	0	10
0	1	0	1	1	→ 1	0	0	0	1	11
0	1	1	0	0	→ 1	0	0	1	0	12
0	1	1	0	1	→ 1	0	0	1	1	13
0	1	1	1	0	→ 1	0	1	0	0	14
0	1	1	1	1	→ 1	0	1	0	1	15
1	0	0	0	0	→ 1	0	1	1	0	16
1	0	0	0	1	→ 1	0	1	1	1	17
1	0	0	1	0	→ 1	1	0	0	0	18
1	0	0	1	1	→ 1	1	0	0	1	19

❑ When binary sum ≤ 1001 , identical binary and BCD

❖ **No conversion needed**

❑ When binary sum > 1001 , non-valid binary corresponds to BCD number.

❖ **Correction required**

❖ Add $(0110)_2$ or $(6)_{10}$ to binary sum for correct BCD representation

❖ This addition produces output carry.

Boolean function for correction:

$$C = K + Z_8 Z_4 + Z_8 Z_2$$

1. $C=0$, no addition to binary sum.


2. $C=1$, add $(0110)_2$ via bottom adder.

BCD Adder

The circuit of the BCD adder will be as shown in the figure.

- When the **Output carry** is equal to **zero**, the correction factor equals zero.

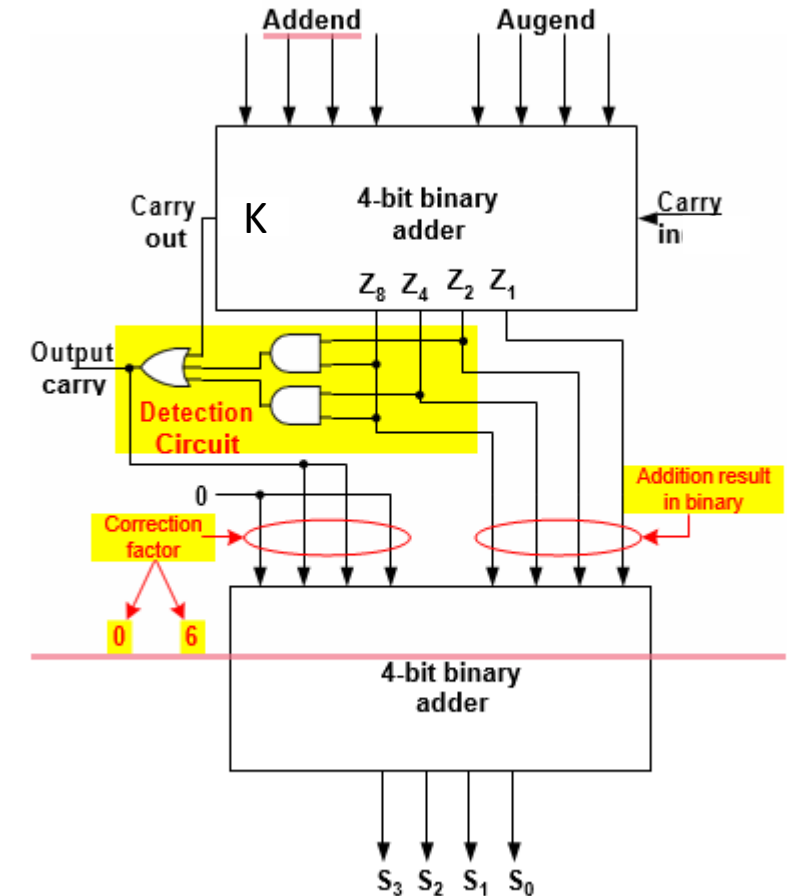When the **Output carry** is equal to **one**, the correction factor is 0110.



2 Bit Magnitude Comparator

2 Bit Magnitude Comparator – A comparator used to compare two binary numbers each of two bits is called a 2-bit Magnitude comparator. It consists of four inputs and three outputs to generate less than, equal to and greater than between two binary numbers. The truth table for a 2-bit comparator is given below:

INPUT				OUTPUT		
A1	A0	B1	B0	A<B	A=B	A>B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

2 Bit Magnitude Comparator

From the above K-maps logical expressions for each output can be expressed as follows

A > B

B1B0 \ A1A0	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	0	1
00	1	1	0	0

A = B

B1B0 \ A1A0	00	01	11	10
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
00	0	0	0	1

A < B

B1B0 \ A1A0	00	01	11	10
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
00	0	0	1	0

$$\mathbf{A > B: A_1 B_1' + A_0 B_1' B_0' + A_1 A_0 B_0'}$$

$$\mathbf{A = B: A_1' A_0' B_1' B_0' + A_1' A_0 B_1' B_0 + A_1 A_0 B_1 B_0 + A_1 A_0' B_1 B_0'}$$

$$: A_1' B_1' (A_0' B_0' + A_0 B_0) + A_1 B_1 (A_0 B_0 + A_0' B_0')$$

$$: (A_0 B_0 + A_0' B_0') (A_1 B_1 + A_1' B_1')$$

$$: (A_0 \text{ Ex-Nor } B_0) (A_1 \text{ Ex-Nor } B_1)$$

$$\overline{A_0 \oplus B_0} \cdot \overline{A_1 \oplus B_1}$$

$$\mathbf{A < B: A_1' B_1 + A_0' B_1 B_0 + A_1' A_0' B_0}$$


2 Bit Magnitude Comparator

By using these Boolean expressions, we can implement a logic circuit for this comparator.

$$A > B = A_1 B_1' + B_0 A_0 B_1' + B_0 A_0 A_1$$


$$A = B = \overline{A_0 \oplus B_0} \cdot \overline{A_1 \oplus B_1}$$
 
$$A < B = B_1 A_1' + B_0 B_1 A_0' + A_1' A_0' B_0$$




Decoder

 - A Decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines



 Consider a vending machine that takes 3 bits as input and releases a single product, out of the available 8 product sort



2-to-4 decoders

Decimal #	Input		Output			
	A_1	A_0	D_0	D_1	D_2	D_3
0	0	0	1	0	0	0
1	0	1	0	1	0	0
2	1	0	0	0	1	0
3	1	1	0	0	0	1

Truth table for 2-to-4 decoder


 
 


Figure 3: Implementation 2-to-4 decoder

3x8 DECODER

- A 3×8 line decoder decodes 3 input bits into one of 8 possible outputs x
- Each output represents one of the minterms of the 3 input variables

Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

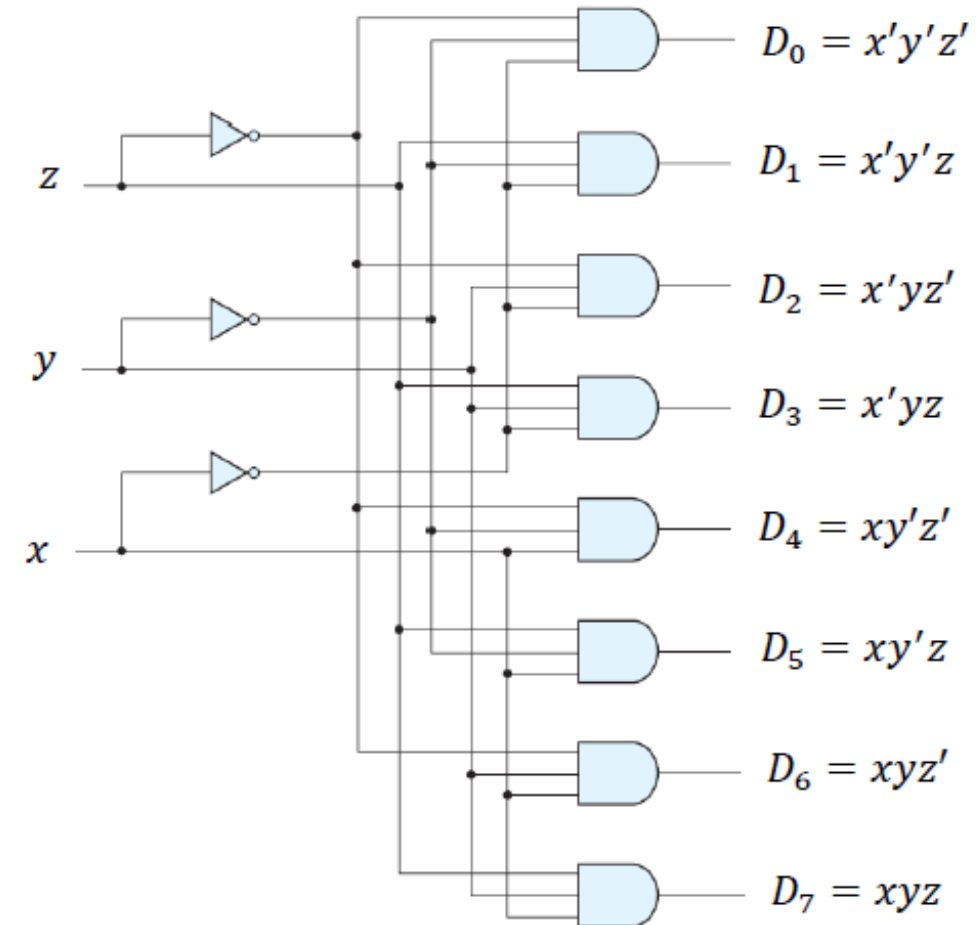

2-to-4 decoder with enable

Decimal value	Enable	Inputs		Outputs			
	E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
	0	X	X	0	0	0	0
0	1	0	0	1	0	0	0
1	1	0	1	0	1	0	0
2	1	1	0	0	0	1	0
3	1	1	1	0	0	0	1

Table 2: Truth table of 2-to-4 decoder with enable

 


Figure 4: Implementation 2-to-4 decoder with enable

Decoder implementation of a Full Adder


Decimal value	Input			Output	
	X	Y	Z	S	C
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

Truth table of the Full Adder

The output functions S & C can be expressed in sum-of-minterms forms as follows:


$$S(X,Y,Z) = \sum(1,2,4,7)$$

$$C(X,Y,Z) = \sum(3,5,6,7)$$

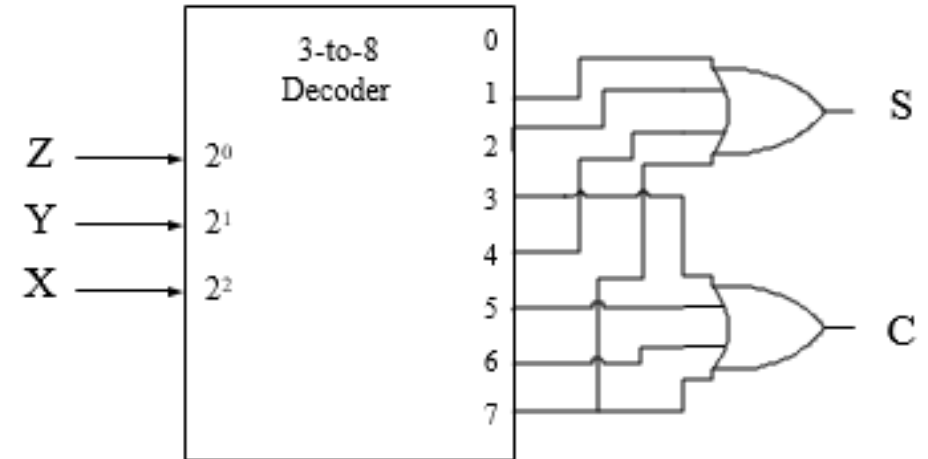


ENCODERS

 - An encoder is a digital circuit that performs the inverse operation of a decoder
- An encoder has 2^n input lines and n output lines
- The output lines generate the binary equivalent of the input line whose value is 1



A typical Encoder

8×3 OCTAL-TO-BINARY ENCODER

 

: Octal-to-binary encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1


Truth table of Octal-to-binary encoder

$$x = D_4 + D_5 + D_6 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$

$D_7 D_6 D_5 D_4 D_3 D_2 D_1 D_0$

 

Major Limitation of Encoders

- Exactly one input must be active at any given time.
- If the number of active inputs is less than one or more than one, the output will be incorrect.

For example, if $D_1 = D_2 = 1$, the output of the encoder $A_1A_0 = 11$, which implies incorrect output.

In the previous example,

if $D_1 = D_2 = 1$, the output corresponding to D_2 will be produced ($A_1A_0 = 10$) since D_2 has higher priority than D_1 .

Major Limitation of Encoders

Two Problems to Resolve.

1. If two or more inputs are active at the same time, *what should the output be?*
2. An output of all 0's is generated in 2 cases:
 - when all inputs are 0
 - when E_0 is equal to 1.

How can this ambiguity be resolved?

Solution To Problem 1:

- Use a *Priority Encoder* which produces the output corresponding to the input with higher priority.

Solution To Problem 2:

- Provide one more output signal V to indicate *validity* of input data.
- $V = 0$ if none of the inputs equals 1, otherwise it is 1

4-to-2 Priority Encoder

	Inputs				Outputs		
	D3	D2	D1	D0	A1	A0	V
1	0	0	0	0	X	X	0
2	0	0	0	1	0	0	1
3	0	0	1	X	0	1	1
4	0	1	X	X	1	0	1
5	1	X	X	X	1	1	1

Truth table of 4-to-2 priority encoder

		D ₁ D ₀			
		00	01	11	10
D ₃ D ₂	00	X	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$A_1 = D_3 + D_2$

		D ₁ D ₀			
		00	01	11	10
D ₃ D ₂	00	X	0	1	1
	01	0	0	0	0
	11	1	1	1	1
	10	1	1	1	1

$A_2 = D_3 + D_1 D'_2$

$$V = D_3 + D_2 + D_1 + D_0$$

 


Figure : Equations and circuit for 4-to-2 priority encoder