

**International Islamic University Chittagong**  
**Department of Electrical and Electronic Engineering**

Final Examination Autumn-2018  
 Course Code: EEE 1101  
 Marks: 50

Program: B.Sc. Engg. (EEE)  
 Course Title: Electrical Circuit-I  
 Time: 2 hours 30 minutes

**PART-A**

[Answer any two questions from the followings; figures in the right margin indicate full marks.]

- 1(a). Why source transformation is used in solving some networks? Do you think that source transformation is applicable when an ideal voltage is connected to a network? Justify your comment using simple example. 02
- 1(b). Use source conversion technique to find the voltage  $v_o$  in the following circuit in Fig. 1. 04

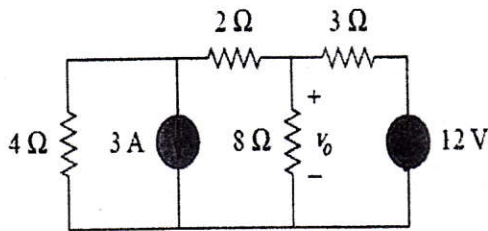


Fig. 1 Figure for question no. 1 (b)

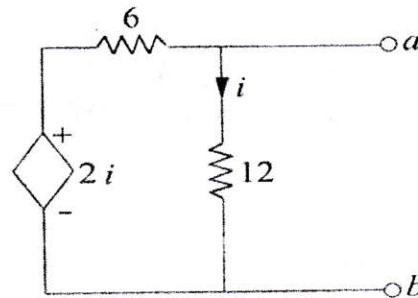


Fig. 2 Circuit for question no. 1 (c)

- 1(c). Find the Thevenin equivalent circuit for the network shown in Fig. 2 which contains only a dependent source. Consider the value of the resistors as ohm. 04
- 2(a). What is maximum power transfer theorem? Derive the condition for transferring maximum power to the load for a linear bilateral network. 05
- 2(b). In the circuit shown in Fig. 3, obtain the condition for maximum power transfer to the load  $R_L$  and determine the maximum power consumed by  $R_L$  (all resistances are in ohm). 05

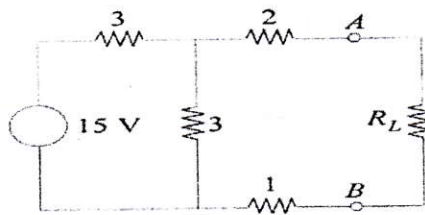


Fig. 3 Circuit for question no. 2 (b)

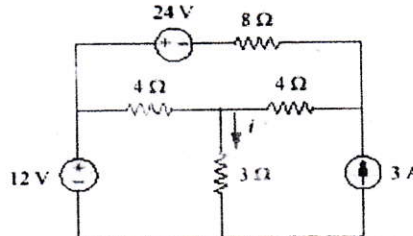


Fig. 4 Circuit for question no. 3 (a)

- 3(a). State superposition theorem. Find  $i$  using superposition theorem from Fig. 4. 05
- 3(b). Find the Norton equivalent circuit for the network shown in Fig. 5 at  $a-b$ . 05

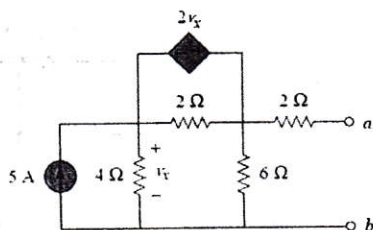


Fig. 5 Circuit for question no. 3 (b)

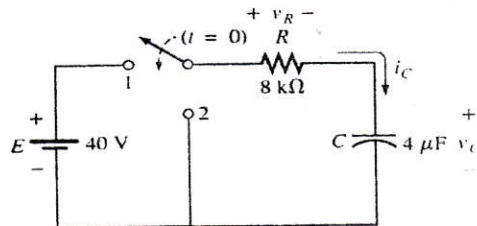


Fig. 6 Circuit for question no. 4 (a)

## PART-B

[Answer any three questions from the followings; figures in the right margin indicate full marks.]

- 4(a). (i) Find the mathematical expressions for the transient behavior of  $v_C$ ,  $i_C$ , and  $v_R$  for the circuit of Fig. 6 when the switch is moved to position 1. Plot the curves of  $v_C$ ,  $i_C$ , and  $v_R$  (ii) How much time must pass before it can be assumed, for all practical purpose, that  $i_C \cong 0$  and  $v_C \cong E$  volts. 05
- 4(b). Three capacitors  $C_1$ ,  $C_2$  and  $C_3$  are connected in series and the corresponding equivalent capacitance is  $C_s$ . Derive the equation for  $C_s$ . 05
- 5(a). Define relative permeability, magnetomotive force, magnetic field intensity and flux density mentioning their units. 04
- 5(b). Which section of Fig. 7 has the largest reluctance to the setting up the flux lines through its longest dimension? And, why? Explain shortly in your own word. 03

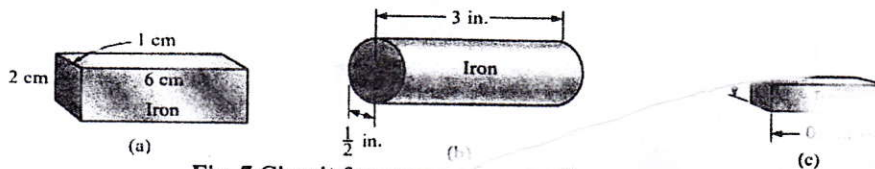


Fig. 7 Circuit for question no. 5 (b)

- 5(c). Classify materials with reference to their magnetic permeability ( $\mu_r$ ). Derive the equation  $B = \mu H$ ; Where the symbols have their usual meaning. 03
- 6(a). For the series magnetic circuit of Fig. 8 i) Find the value of  $I$  required to develop a magnetic flux  $\Phi = 4 \times 10^{-4}$  Wb. ii) Determine  $\mu$  and  $\mu_r$  for the material under these conditions. 05

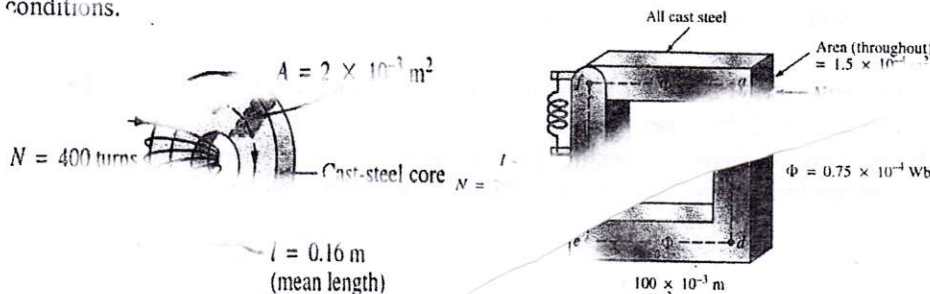


Fig. 8 Figure for question no. 6 (a) Figure for question no. 6 (b)

- 6(b). Find the value of  $I$  required to establish a magnetic flux of  $\Phi$  in the magnetic circuit of Fig. 8 (b). 05
- 7(a). Find the voltage across and charge on each capacitor of the network of Fig. 10 after each has charged up to its steady state value. 05

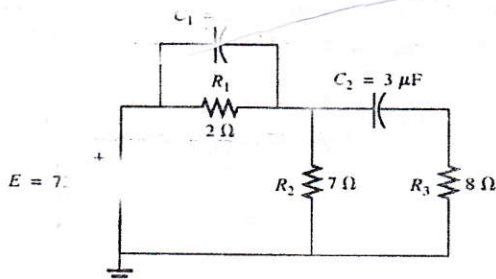


Fig. 10 Figure for question no. 7 (a)

- 7(b). Describe ampere's circuital law. Compare between magnetic and electric circuits mentioning the analogous variables. 05