

Operational Amplifier (OP-Amp)


Definition:

The operation amplifier is a versatile device that can be used to amplify dc as well as ac input signals and was originally designed for performing mathematical operations such as addition, subtraction, multiplication, integration and differentiation.

Operational amplifier can:

- amplify dc and ac signals.
- Perform some mathematical operations:-
 - Addition
 - Subtraction
 - Multiplication
 - Integration &
 - Differentiation.

Symbol of op-amp

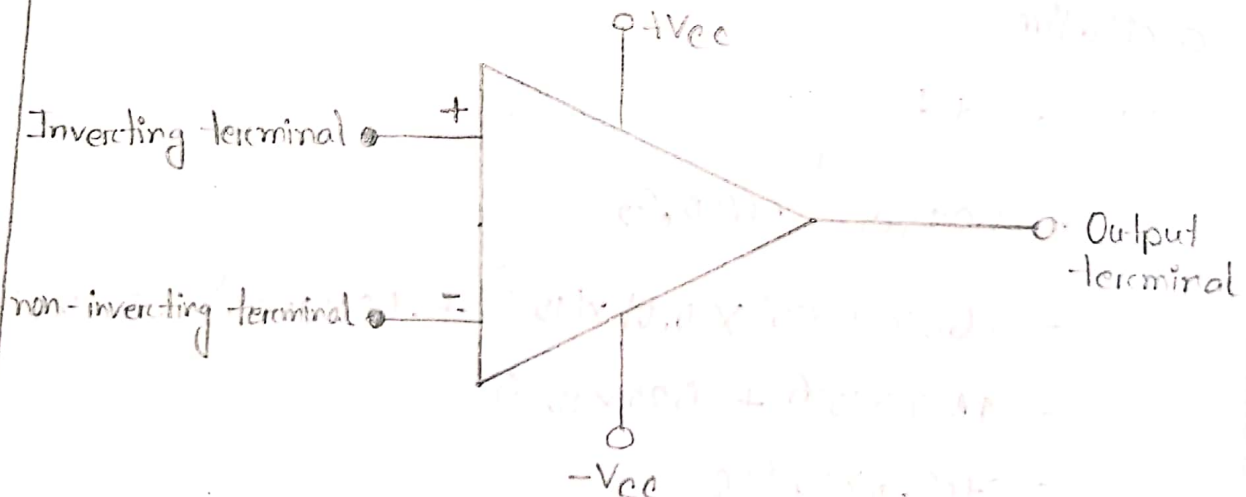

Life/Biasing voltage \rightarrow main thing.


IC (Op-amp):-

741.


offset Voltage: Biasing voltage এর কারণে input ছাড়াই যে Output Voltage আসে, তাকে সেই পরিমাণ Voltage ফিন্ন Output 0 হয়, তাকে D.V বলে,

offset Voltage-টি অকমার্শে Positive অথবা negative হতে পারে,

Input Resistance:-

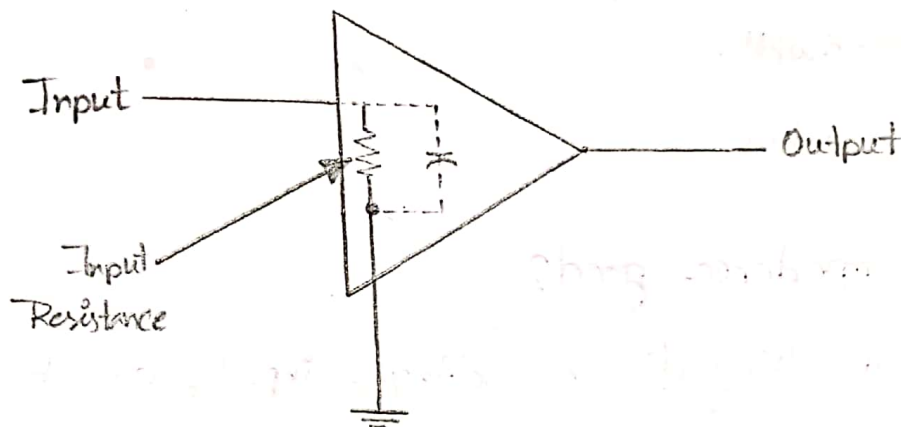

Output Resistance:

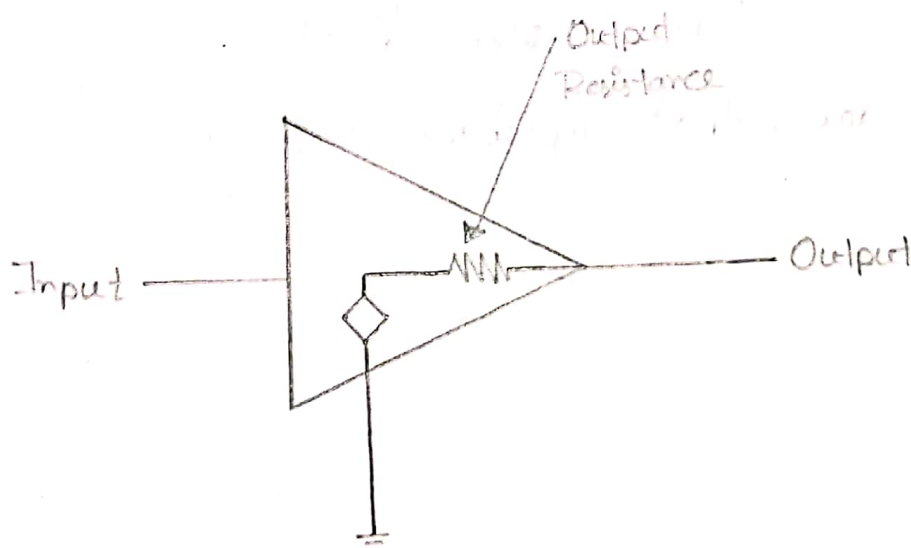

Characteristics of an ideal op-amp:

- \Rightarrow Infinite voltage gain.
- \Rightarrow Input impedance infinite.
- \Rightarrow Output impedance zero.
- \Rightarrow input no voltage.
- \Rightarrow Output zero voltage.
- \Rightarrow from D.C. to the highest A.C.
- \Rightarrow infinite bandwidth.
- \Rightarrow Slope rate infinite.


• Why is high impedance good?

\Rightarrow It is a good thing for a voltage input, as if the input impedance is high ~~as~~ compared to the source impedance then the voltage level will not drop too much due to the divider effect.


• Why is low output impedance is good?

\Rightarrow


Divider effect:-

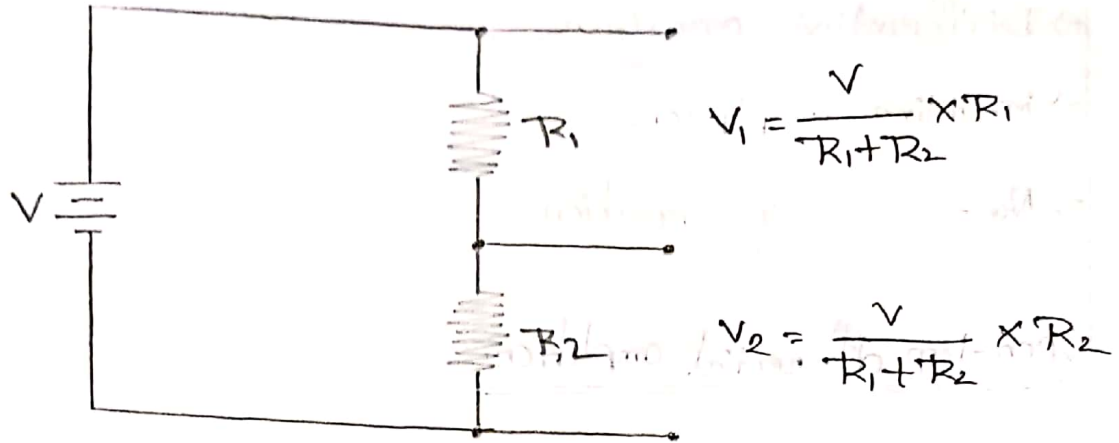

Equivalent Circuit of an op-amp:-

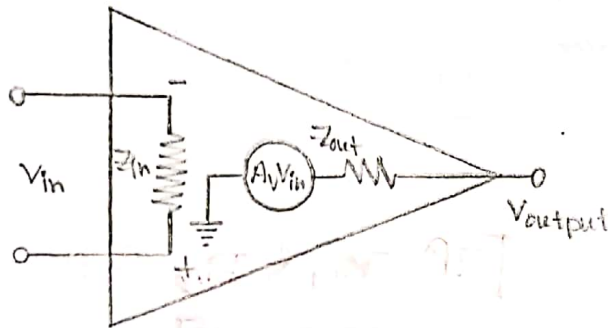

Practical Op-amp

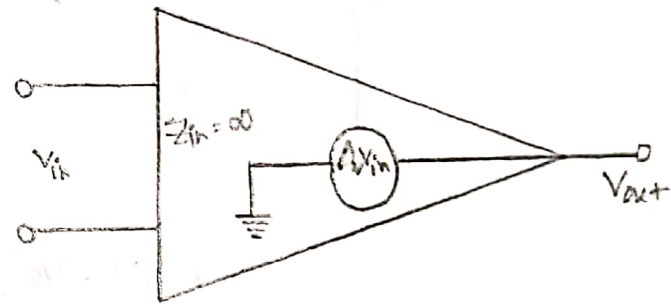

ideal op-amp

- inverting and non-inverting terminal as difference input शिफ़र (विध), which is V_{id} .
- V_{id} amplity A_{vid} V_{id} V_{out} .
- V_{out} output शिफ़र V_{out} V_{out} .

Open-loop op-amp configuration:


There are three open-loop op-amp configurations:

=> Differential amplifier

=> inverting amplifier

=> Non-inverting amplifier

Open-loop differential amplifier:

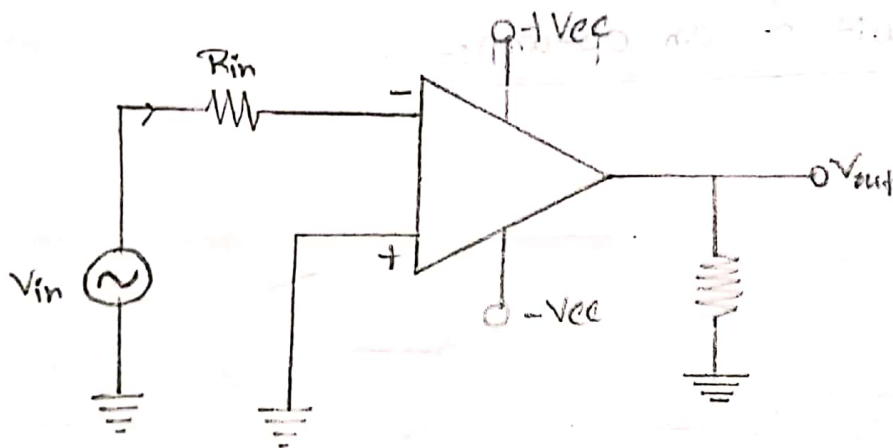

$$V_{out} = A (V_1 - V_2)$$

$$V_{out} = A (V_{in1} - V_{in2})$$

↓

Open loop voltage gain


$$= A (0 - V_{in2})$$

$$= -A V_{in2}$$

[If R_{in1} & $R_{in2} \cong 0$

অনেক সময়]

Open-loop non-inverting amplifier:

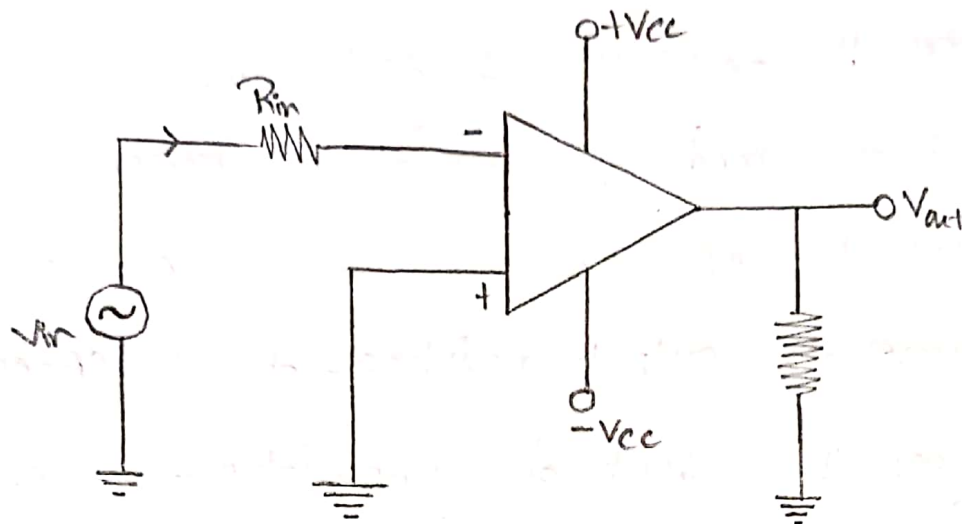

$$V_{out} = A(V_1 - V_2)$$


$$V_{out} = A(V_{in1} - V_{in2})$$

$$V_{out} = A(V_{in} - 0)$$


$$V_{out} = AV_{in}$$

Feedback:-

• Positive feedback

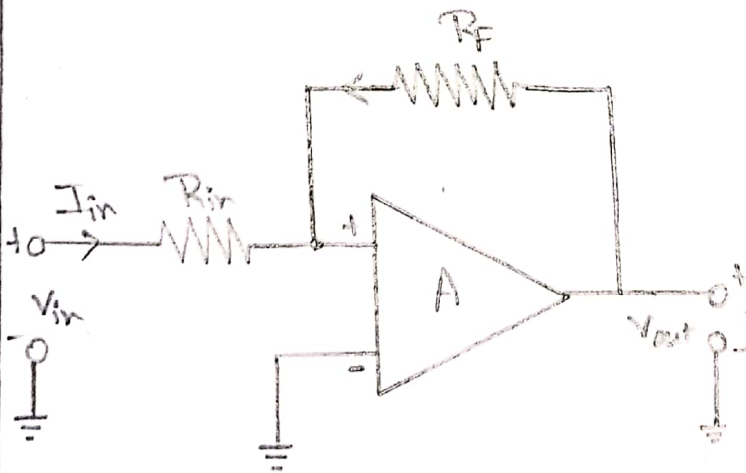


• Negative feedback

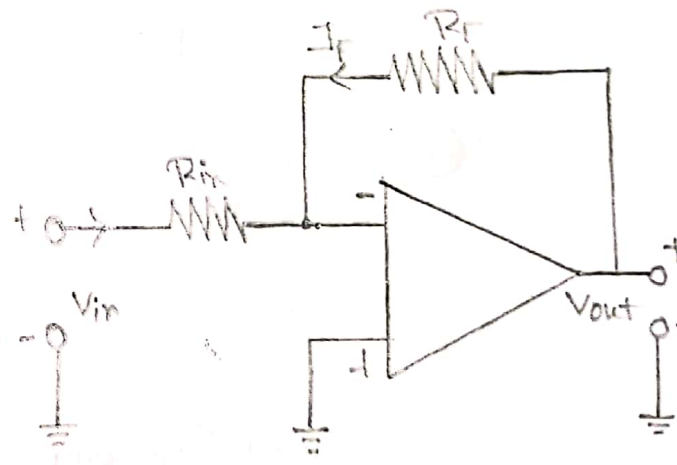

Advantages of negative feedback:-


- ⇒ It reduces the gain and makes it controllable
- ⇒ It reduces the possibility of distortion.
- ⇒ It reduces the bandwidth i.e. frequency range.
- ⇒ It increases the input resistance of the op-amp.
- ⇒ It decreases the output resistance of the op-amp.
- ⇒ It reduces the effect of temperature, power supply on the gain of the circuit.

Gain of OP-amp Configuration:-

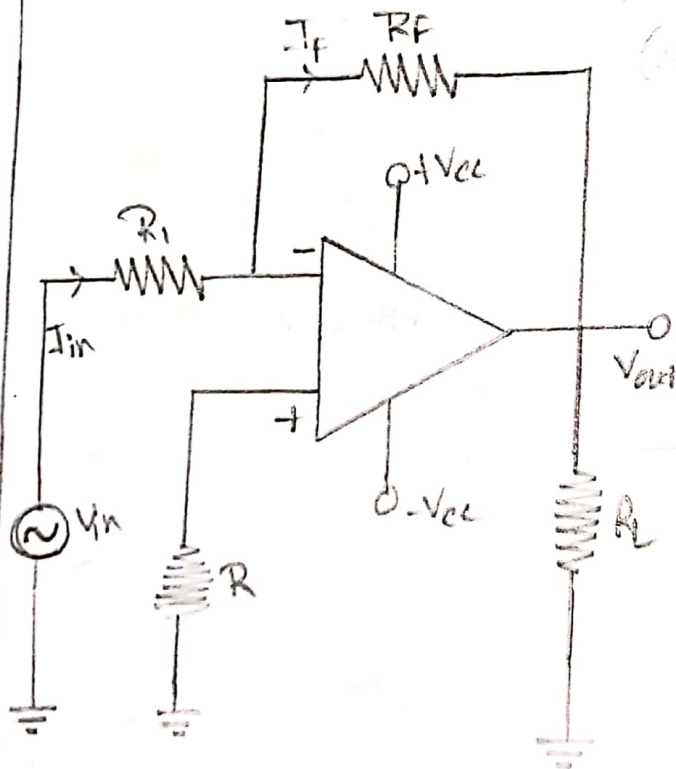

inverting amplifier

$$A_F = -\frac{R_F}{R_1}$$

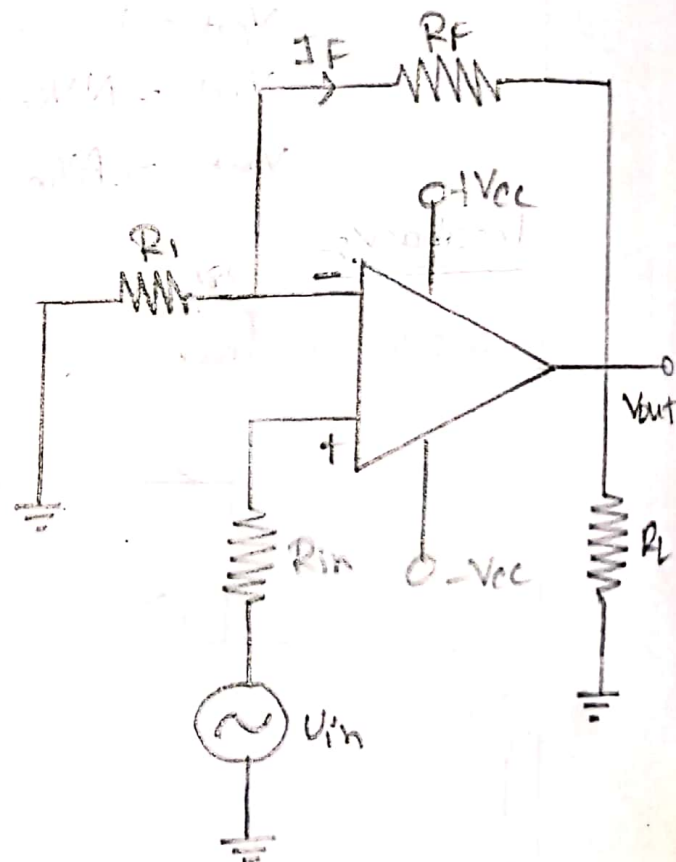

Non-inverting amplifier

$$A_F = 1 + \frac{R_F}{R_1}$$

Gain of an inverting amplifier:-

$I_B \approx 0$ [In current is very small, feedback

$I_{in} = I_B + I_P$ A (input current (I_P) is very small, I_B is negligible, so $I_{in} = I_P$]

$$I_{in} = I_P$$

$$I_P = \frac{V_2 - V_0}{R_P}$$

$$I_{in} = \frac{V_{in} - V_2}{R_1}$$

$$V_0 = A(V_1 - V_2)$$

$$\Rightarrow V_0 = A(0 - V_2)$$

$$\Rightarrow V_0 = -AV_2$$

$$\Rightarrow V_2 = \frac{-V_0}{A}$$

We know,

$$I_P = I_{in}$$

$$\Rightarrow \frac{V_2 - V_{out}}{R_F} = \frac{V_{in} - V_2}{R_1}$$

$$\Rightarrow \frac{\frac{-V_0}{A} - V_{out}}{R_F} = \frac{V_{in} + \frac{V_0}{A}}{R_1}$$

$$\Rightarrow V_{in} R_F + \frac{V_0}{A} R_F = -\frac{V_0}{A} R_1 - V_{out} R_1$$

$$\Rightarrow V_{in} R_F = \frac{-V_{out}}{A} R_1 - V_{out} R_1 - \frac{V_{out}}{A} R_F$$

$$\Rightarrow V_{in} R_F = -V_{out} \left(\frac{R_1}{A} + R_1 + \frac{R_F}{A} \right)$$

$$\Rightarrow \frac{V_{in}}{V_{out}} R_F = -\frac{R_1 + R_1 A + R_F}{A}$$

$$\Rightarrow \frac{V_{in}}{V_{out}} = -\frac{R_1 + R_1 A + R_F}{A R_F}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -\frac{A R_F}{R_1 + R_1 A + R_F}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -\frac{A R_F}{A R_1} \quad [\text{since } A R_1 \gg R_1 + R_F]$$

Therefore,

$$A_p = \frac{-R_F}{R_1}$$

A Gain of a non-inverting amplifier:

$$V_{out} = A(V_{in} - 0) \Rightarrow A = \frac{V_{out}}{V_{in}}$$

$$V_{out} = A(V_1 - V_2)$$

$$V_1 = V_{in} [R_{in} \approx 0]$$

$$V_2 = V_f$$

$$= \frac{V_{out}}{R_1 + R_f} \times R_1$$

$$= \frac{R_1}{R_1 + R_f} \times V_{out}$$

$$V_{out} = A V_{in} - \left(\frac{A R_1}{R_1 + R_f} \right) V_{out}$$

$$\Rightarrow V_{out} + \frac{A R_1}{R_1 + R_f} V_{out} = A V_{in}$$

$$\Rightarrow \frac{R_1 + R_f + A R_1}{R_1 + R_f} \times V_{out} = A V_{in}$$

$$\Rightarrow V_{out} = \frac{A V_{in} (R_1 + R_f)}{R_1 + R_f + A R_1}$$

$$\Rightarrow V_{out} = \frac{A (R_1 + R_f) V_{in}}{R_1 + R_f + A R_1}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A (R_1 + R_f)}{R_1 + R_f + A R_1}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A R_1 + R_f}{A R_1}$$

$$\therefore \frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_1}$$