

Name: Ezaz Ahmed

ID : C223009

Section: 2AM

Assignment


Ex: 25.1 - A differential amplifier has an open-circuit voltage gain 100. The input signals are 3.25 V and 3.15 V. Output voltage?

Solution:

$$\begin{aligned}\text{Output voltage, } V_o &= A(V_1 - V_2) \\ &= 100(3.25 - 3.15) \quad [\text{Given in the ques}] \\ \therefore V_o &= 10 \text{ V.}\end{aligned}$$

Ans:

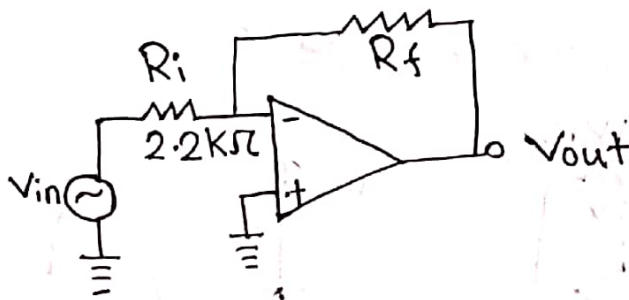Ex: 25.25 - Given the OP-amp configuration. Determine the value of R_f required to produce a closed-loop voltage gain of -100.



Solution:


$$\begin{aligned}A_{CL} &= -\frac{R_f}{R_i} \quad \text{or, } R_f = -A_{CL} \cdot R_i \\ &= -(-100) \cdot (2.2)\end{aligned}$$

$$\therefore R_f = 220 \text{ k}\Omega$$

Ans:

Ex: 25.26-

Output voltage ?

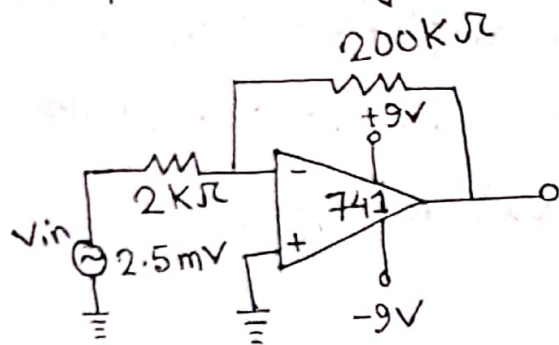

Solution:


$$A_{CL} = -\frac{R_f}{R_i} = -\frac{200 \text{ k}\Omega}{2 \text{ k}\Omega} = -100$$

$$V_{out} = A_{CL} \times V_{in} = (-100) \times (2.5 \text{ mV}) = -250 \text{ mV}$$

$$\therefore V_{out} = -0.25 \text{ V}$$

Ans:

Example: 25.27- output voltage ?

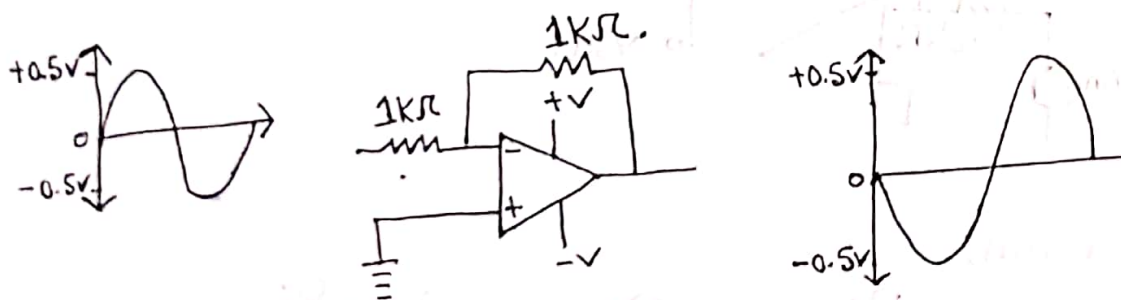


Solution:

$$A_{CL} = -\frac{R_f}{R_i} = -\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega} = -1$$

As A_{CL} is -1 the output will have the same amplitude but with 180° phase inversion.

Ans:

Ex: 28: Output voltage?

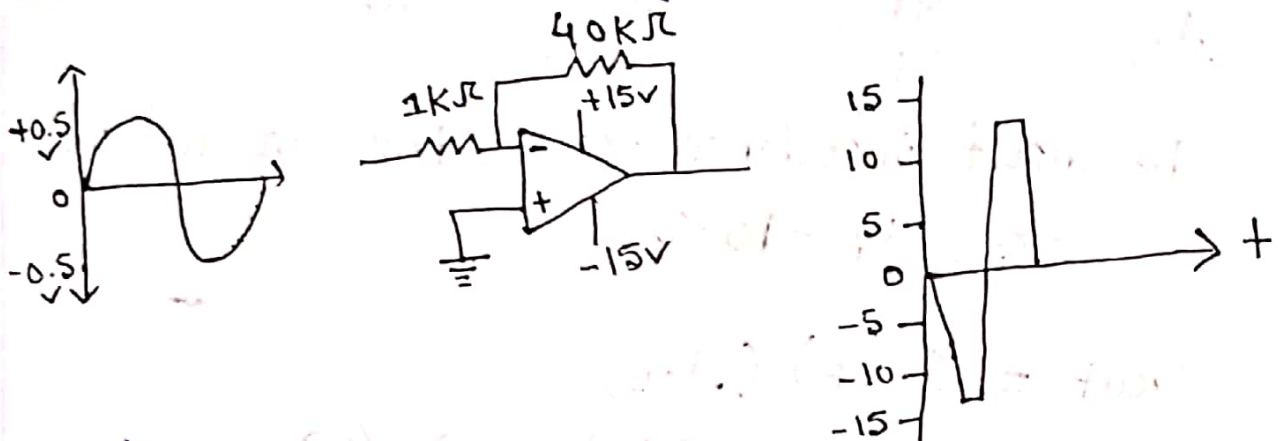


Solution:

$$A_{CL} = - \frac{R_f}{R_i} = - \frac{40\text{k}\Omega}{1\text{k}\Omega} = -40$$

Since supply voltages are $\pm 15\text{V}$ the saturation occurs at $\pm 13\text{V}$. Since the output voltage far exceeds the saturation level, the OP-amp will be driven to deep saturation and it will behave as a non-linear amplifier. This means the output will not have the same shape as input but will clip at the saturation voltage. Note that 180° phase inversion does occur.

Ex: 29-

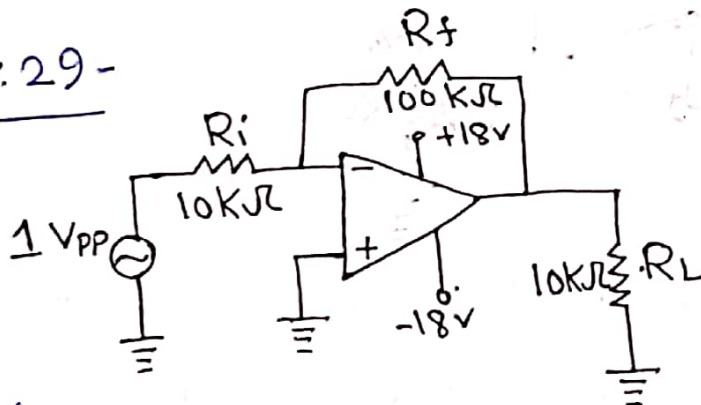

Find:

① closed-loop voltage gain ② input impedance of the circuit ③ maximum operating frequency. Slew rate $0.5\text{V}/\mu\text{s}$

Solution:

i) $A_{CL} = - \frac{R_f}{R_i} = - \frac{100K\Omega}{10K\Omega} = -10$

ii) The input impedance Z_i of the circuit is
 $Z_i \approx R_i = 10K\Omega$

iii) $V_{out} = (1V_{PP})(A_{CL})$
 $= 1V_{PP} \times (-10) = 10V_{PP}$

Peak output voltage is,


$$V_{PK} = 10/2 = 5V$$

$$\therefore f_{max} = \frac{\text{Slew rate}}{2\pi V_{PK}} = \frac{0.5V/\mu s}{2\pi \times 5}$$

$$= \frac{500KHz}{2\pi \times 5} = 15.9KHz$$

Ans:

Ex: 25.31-

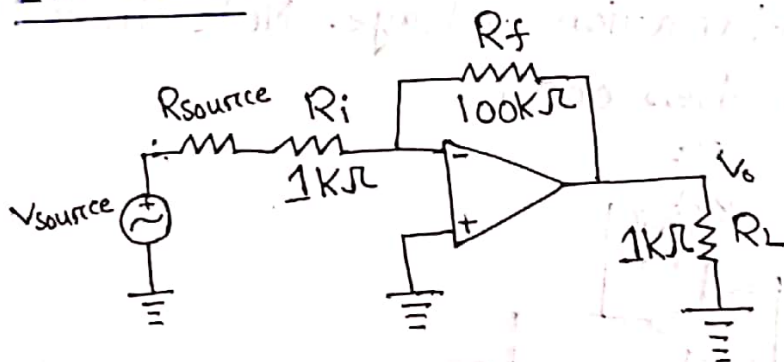

Inverting OP-amp. Find the closed loop gain

if i) $R_{source} = 0\Omega$ ii) $R_{source} = 1\Omega$


Solution:

i) When $R_{\text{source}} = 0 \Omega$; $A_{CL} = -\frac{R_f}{R_i} = -\frac{100k\Omega}{1k\Omega} = -100$

ii) When $R_{\text{source}} = 1k\Omega$; $A_{CL} = -\frac{R_f}{R_{\text{source}} + R_i} = -\frac{100k\Omega}{1k\Omega + 1k\Omega} = -50$

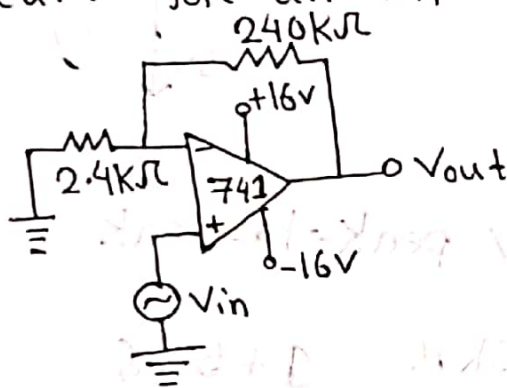Example: 25.32 -

output voltage from non-inverting amplifier circuit for an input of $120 \mu V$




Solution:

$$A_{CL} = 1 + \frac{R_f}{R_i} = 1 + \frac{240k\Omega}{2.4k\Omega} = 1 + 100 = 101$$

$$V_{out} = A_{CL} \times V_{in} = (101) \times (120 \mu V) = 12.12 mV$$

Ex: 25.33 -

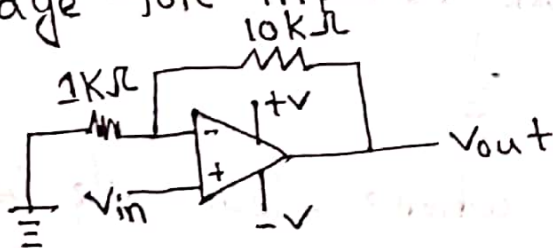non-inverting amplifier circuit find output voltage for input voltage of i) $1V$, ii) $-1V$




Solution:

i) For $V_{in} = 1V$; $V_{out} = A_{CL} \times V_{in} = 11 \times 1V = 11V$

ii) For $V_{in} = -1V$; $V_{out} = A_{CL} \times V_{in} = 11 \times (-1V) = -11V$

Ex-25.34; Peak-to-peak output voltage ?

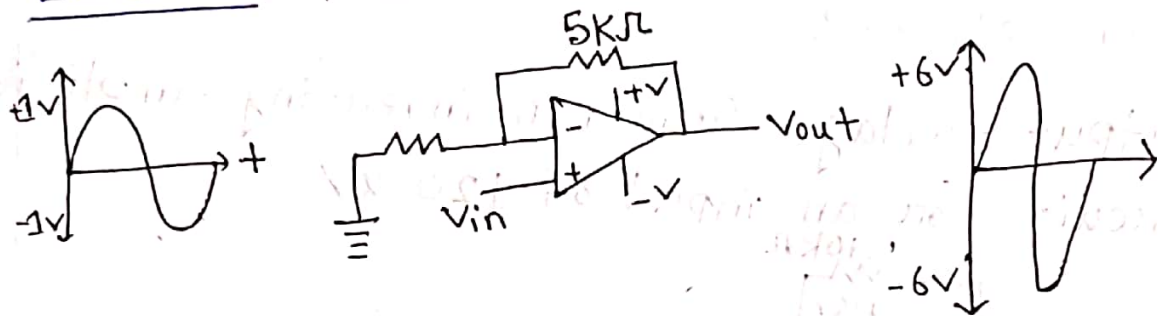


Solution:

The input signal is 2V peak-to-peak

$$A_{CL} = 1 + \frac{R_f}{R_i} = 1 + \frac{5K\Omega}{1K\Omega} = 1 + 5 = 6$$

Peak-to-peak output voltage = $6 \times 2 = 12V$

Ex-25.35:

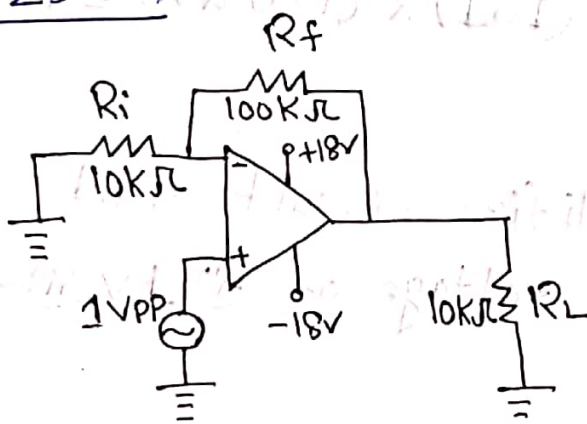

i) $A_{CL} = ?$ ii) f_{max} where slew rate is $0.5V/\mu s$

Solution:

$$\textcircled{i} A_{CL} = 1 + \frac{R_f}{R_i} = 1 + \frac{100K\Omega}{10K\Omega} = 1 + 10 = 11$$

$$\textcircled{ii} V_{out} = A_{CL} \times V_{in} \\ = 11 \times (1 V_{PP}) = 11 V_{PP}$$

$$V_{PK} = 11/2 = 5.5V$$


$$f_{max} = \frac{0.5V/\mu s}{2\pi \times 5.5} = 14.47 KHz \quad [\because 0.5V/\mu s = 500 KHz]$$

$$\therefore f_{max} = 14.47 KHz$$

Ex

25.44:

output voltage for summing amplifier?

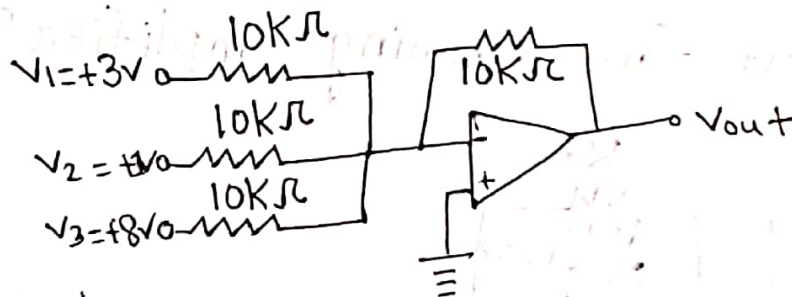


Solution:

$$V_{out} = -(V_1 + V_2 + V_3) = -(3 + 1 + 8) = -12V$$

Ans:

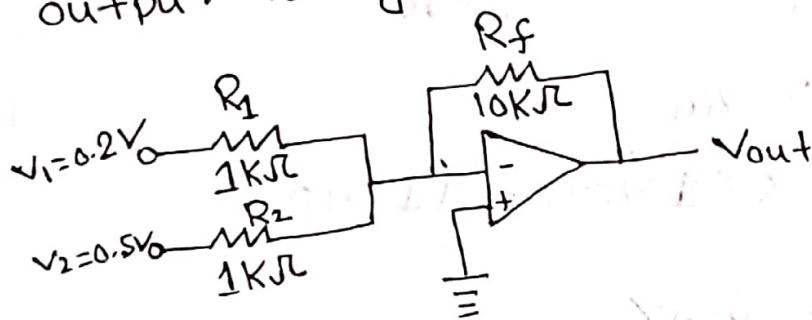Ex: 25.45-
output voltage for summing amplifier?



Solution:


$$R_f = 10\text{K}\Omega, R_1 = R_2 = R = 1\text{K}\Omega$$

gain of the amplifier $= -\frac{R_f}{R} = -\frac{10\text{K}\Omega}{1\text{K}\Omega} = -10$

$$\text{Now, } V_{out} = -\frac{R_f}{R}(V_1 + V_2) = -\frac{10\text{K}\Omega}{1\text{K}\Omega}(0.2 + 0.5)$$

$$= -7\text{V}$$

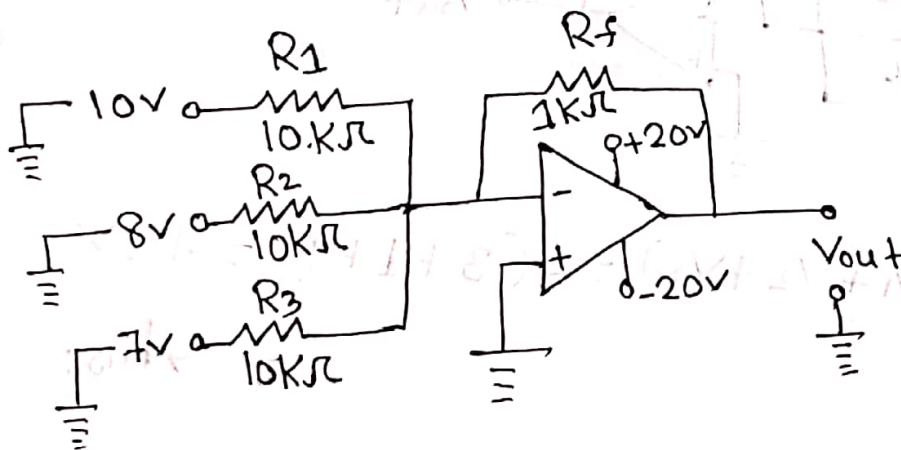Ex: 25.46- V_{out} for summing amplifier?



Solution:

$$\text{gain of amplifier} = -\frac{R_f}{R} = -\frac{1\text{K}\Omega}{10\text{K}\Omega} = -\frac{1}{10}$$

$$V_{out} = - \frac{R_f}{R} (V_1 + V_2 + V_3)$$


$$\therefore V_{out} = - \frac{1k\Omega}{10k\Omega} (10 + 8 + 7) = -2.5V$$

Ans:

Ex: 25.48:

V_{out} for each combinations -

V_1	V_2	V_3
+10	0	+10
0	+10	+10
+10	+10	+10

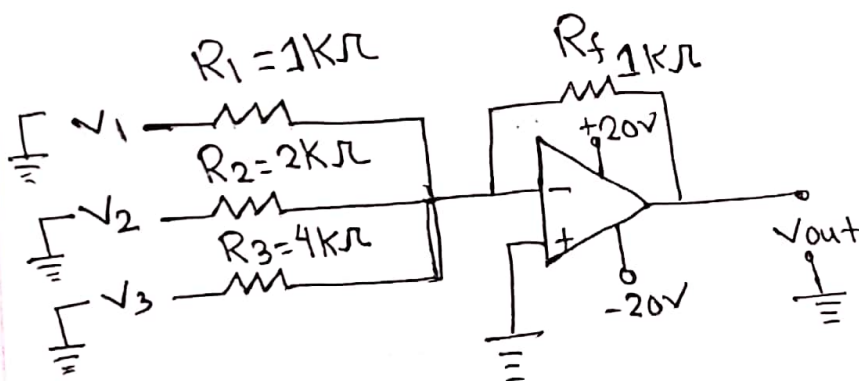

Solution:

$$V_{out} = - \left(\frac{1k\Omega}{1k\Omega} V_1 + \frac{1k\Omega}{2k\Omega} V_2 + \frac{1k\Omega}{4k\Omega} V_3 \right)$$

$$V_{out} = - (V_1 + 0.5V_2 + 0.25V_3)$$

$$\text{for first set, } V_{out} = - (10 + 0.5 \times 0 + 0.25 \times 10) = -12.5V$$

for second set, $V_{out} = -(0 + 0.5 \times 10 + 0.25 \times 10)$
 $= -7.5V$

for third set, $V_{out} = -(10 + 0.5 \times 10 + 0.25 \times 10)$
 $= -17.5V$

Ans:

0V	10V	0V
011	0	011
011	011	0
011	011	011



$V_{out} = -\left(\frac{R_f}{R_1} \cdot V_1 + \frac{R_f}{R_2} \cdot V_2 + \frac{R_f}{R_3} \cdot V_3\right)$

for first set, $V_{out} = -\left(\frac{10k}{10k} \cdot 10 + \frac{10k}{20k} \cdot 10 + \frac{10k}{40k} \cdot 10\right)$

$= -(10 + 5 + 2.5) = -17.5V$