

Important Ques:

- (i) Working principle of n-p-n transistor.
- (ii) Common emitter circuit and its input output characteristics.
- (iii) How transistor acts as an amplifier.
- (iv) Transistor 3 region and transistor can act as a switch and amplifier. (v) α and β relation.

Article:


8.6, 8.8, 8.9, 8.12, 8.22

Math:

8.1-8.12

Book: Principles of electronics
(V.K. Mehta)


Working principle of n-p-n transistor:

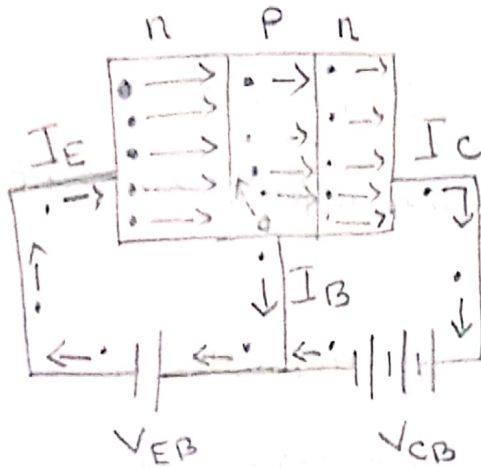

This is a npn transistor with forward bias to emitter-base junction and reverse bias to collector-base junction. The forward bias causes the electrons in the n-type emitter to flow towards the base. This constitutes the emitter current I_E . As these electrons flow through the p-type base, they tend to combine with the holes. As the base is lightly doped and very thin therefore only a few electrons combine with holes to constitute base current I_B . The remainder cross over into the collector region to constitute collector current I_C . In this way, almost the entire emitter current flows in the collector circuit.

$$I_E = I_C + I_B$$

Relation of α and β :

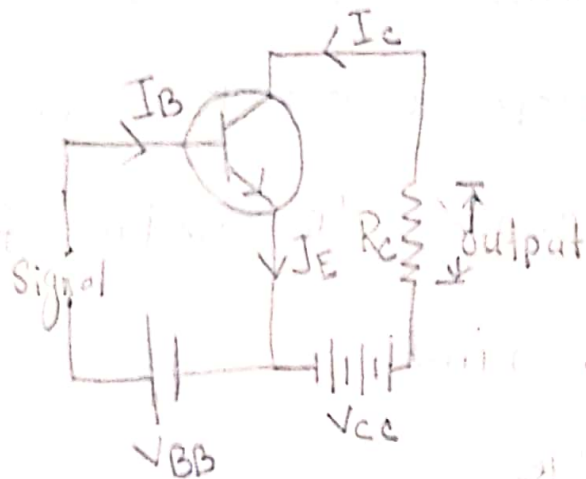

input current is I_B , output current is I_C .

The ratio of change in collector current (ΔI_C) to the change in base current (ΔI_B) is known as base current amplification factor.

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad \text{--- (i)}$$

We know,

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \text{--- (ii)}$$

Now, $I_E = I_B + I_C$ or, $\Delta I_E = \Delta I_B + \Delta I_C$


$$\therefore \Delta I_B = \Delta I_E - \Delta I_C$$

Putting value of ΔI_B in (i):


$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C} = \frac{\frac{\Delta I_C}{\Delta I_E}}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{\alpha}{1 - \alpha}$$

$$\therefore \beta = \frac{\alpha}{1 - \alpha}$$

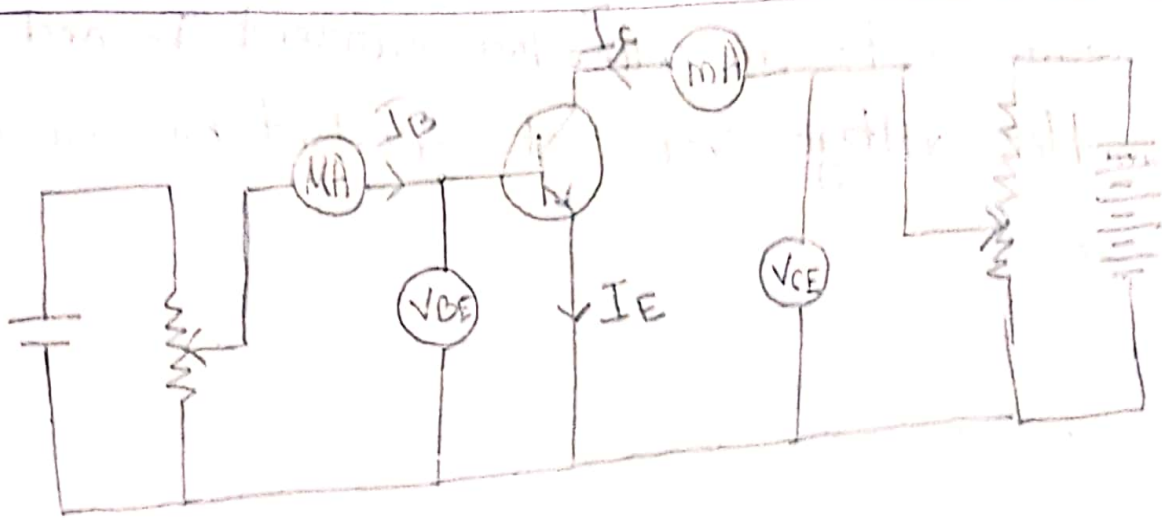Characteristics of common-emitter connection:



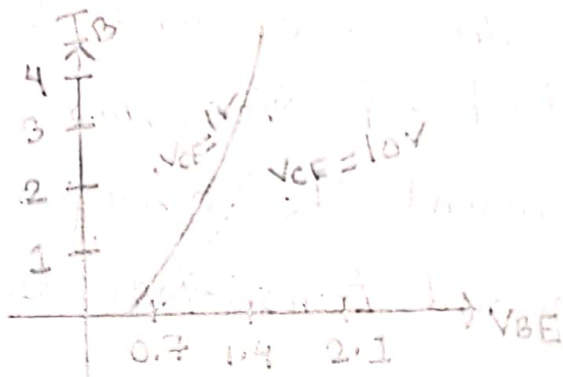Input Characteristics: It is the curve between base current I_B and base-emitter voltage V_{BE} at constant collector-emitter voltage V_{CE} .




⊕ The input characteristics of a CE connection can be determined by the circuit drawn, keeping V_{CE} constant. The characteristics resemble that of a forward biased diode curve. As compared to CB arrangement I_B increases less rapidly with V_{BE} . Input resistance of a CE circuit is higher than that of CB circuit.

$$\text{Input resistance } r_i = \frac{\Delta V_{BE}}{\Delta I_B}$$

Output Characteristics:

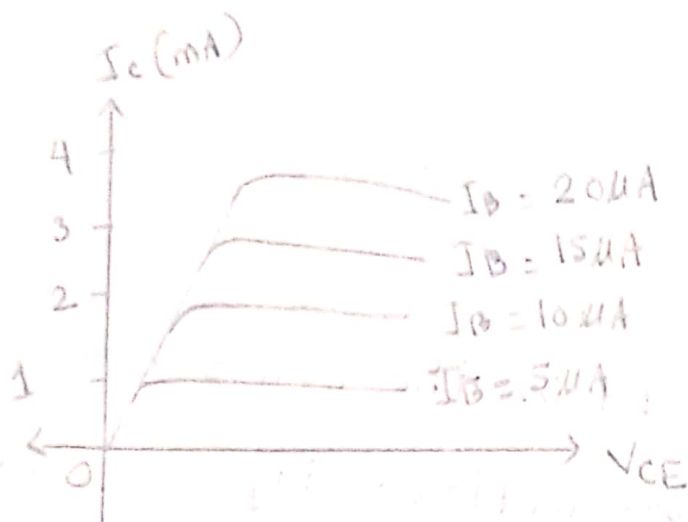
It is the curve between collector current I_c and collector emitter voltage V_{CE} at constant base current I_B .



The collector current I_c varies with V_{CE} between 0 and 1V only. After this ~~the~~ collector current becomes almost constant and independent of V_{CE} . This value of V_{CE} up to which collector current I_c changes with V_{CE} is called knee voltage and transistors work above it. $I_c \approx \beta I_B$, for any value of V_{CE} above knee voltage.



Output resistance $r_o = \frac{\Delta V_{CE}}{\Delta I_c}$ at I_B constant.

Transistor as an Amplifier:

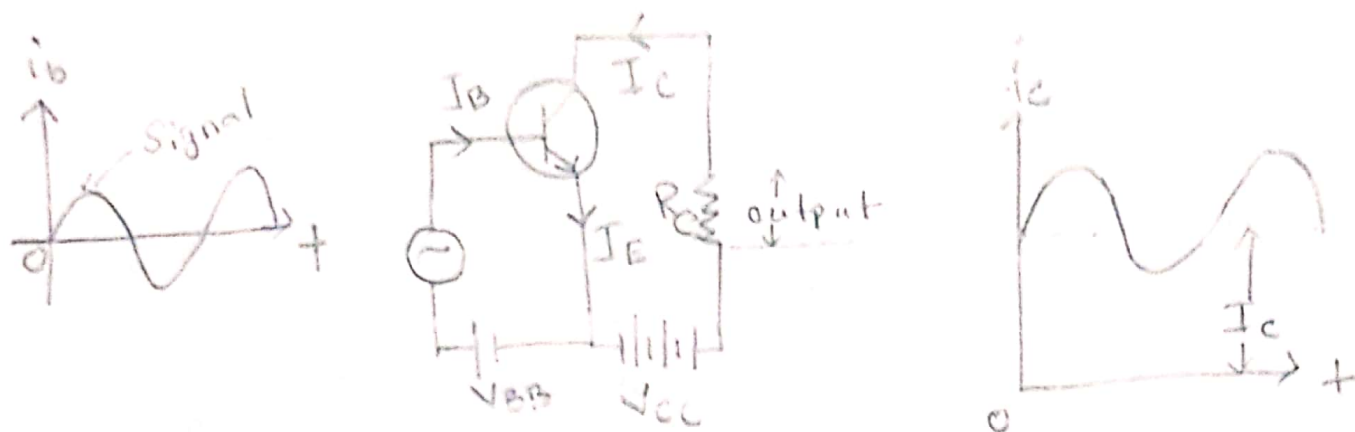

During the positive half-cycle of the signal, the forward bias across the emitter-base junction is increased. Therefore more electrons flow from the emitter to the collector via the base. This causes an increase in the collector current I_C . It produces a greater voltage drop across the collector load resistance R_C . During the negative half cycle of the signal collector current decreases. This results in the decreased output voltage. Hence an amplified output is obtained across the load.

Transistor 3 regions:

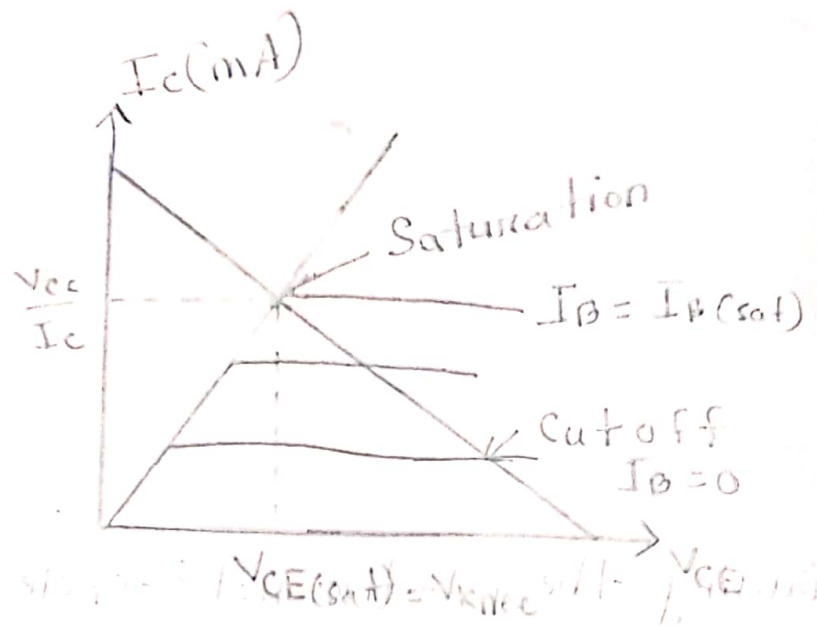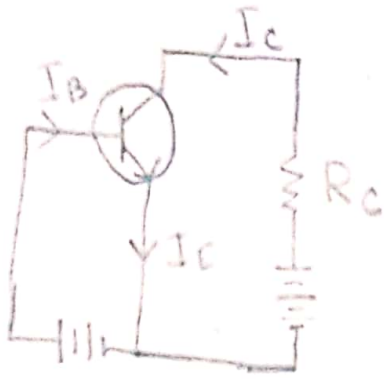

(i) Cut off: The point where the load line intersects the $I_B = 0$ curve is known as cut off. At this point $I_B = 0$ and only a small collector current exists. The collector-emitter voltage is nearly equal to V_{CC} .

$$V_{CE(\text{cut off})} = V_{CC} \quad (\text{Emitter diode and collector diode are off})$$

(ii) Saturation: The point where the load line intersects the $I_B = I_B(\text{sat})$ curve is called saturation. At this point the base current is maximum and so the collector current.

$$I_{C(\text{sat})} \approx \frac{V_{CC}}{R_C}; \quad V_{CE} = V_{CE(\text{sat})} = V_{K_{EE}}$$

(Emitter diode and collector diode on)

(iii) Active region: The region between cut off and saturation is called active region. Collector-base junction

remains reverse biased while base-emitter junction stays forward biased. The transistor will function normally. (Emitter diode is ON and collector diode is OFF)

In saturation the transistor ~~works~~^{act} as ~~an~~ a switch.

In active region the transistor ~~works~~^{act} as an amplifier.

So a transistor can ~~work~~ act both switch and amplifier.

Example 8.1: A common base transistor amplifier has an input resistance of 20Ω and output resistance of $100k\Omega$. The collector load is $1k\Omega$. If a signal of $500mV$ is applied between emitter and base, find the voltage amplification. Assume α_{ac} to be nearly one.

Solution:

$$\text{Input current } I_E = \frac{\text{Signal}}{R_{in}} = \frac{500mV}{20\Omega} = 25mA$$

Since, α_{ac} is nearly 1, output current $I_C = I_E = 25mA$

$$\text{Output voltage } V_{out} = I_C R_C = 25mA \times 1k\Omega = 25V$$

$$\text{Voltage amplification } A_v = \frac{V_{out}}{\text{Signal}} = \frac{25mV}{500mV} = 50$$

Ans:

Example 8.2: In a common base connection $I_E = 1mA$, $I_C = 0.95mA$. Calculate the value of I_B .

Solution: Using the relation, $I_E = I_B + I_C$

$$\text{or, } I_B = I_E - I_C$$

$$= 1 \text{ mA} - 0.95 \text{ mA}$$

$$\therefore I_B = 0.05 \text{ mA}$$

Ans:

Example 8.3 - In a common base connection, current amplification factor is 0.9. If the emitter current is 1 mA, determine the value of base current.

Solution:

$$\text{Here, } \alpha = 0.9, I_E = 1 \text{ mA}$$

$$\text{Now, } \alpha = \frac{I_C}{I_E} \quad \text{or, } I_C = \alpha I_E = 0.9 \times 1 = 0.9 \text{ mA}$$

$$\therefore I_C = 0.9 \text{ mA}$$

$$\text{Again, } I_E = I_B + I_C \quad \text{or, } I_B = I_E - I_C = (1 - 0.9) \text{ mA} \\ = 0.1 \text{ mA}$$

$$\therefore I_B = 0.1 \text{ mA}$$

Ans:

Example 8.4: In a common base connection $I_C = 0.95 \text{ mA}$ and $I_B = 0.05 \text{ mA}$. Find the value of α .

Solution: $I_E = I_B + I_C = 0.05 \text{ mA} + 0.95 \text{ mA} = 1 \text{ mA}$

$$\therefore \alpha = \frac{I_C}{I_E} = \frac{0.95 \text{ mA}}{1 \text{ mA}} = 0.95 \quad \text{Ans:}$$

Example 8.5: In a common base connection the emitter current is 1mA . If the emitter circuit is open, the collector current is $50\mu\text{A}$. Find the total collector current $\alpha = 0.92$

Solution:

Here, $I_E = 1\text{mA}$, $\alpha = 0.92$, $I_{CBO} = 50\mu\text{A}$

\therefore Total collector current, $I_C = \alpha I_E + I_{CBO}$

$$= 0.92 \times 1 + 50 \times 10^{-3}$$


$$= 0.97\text{mA}$$

Ans:

Example 8.6:- In a common base connection $\alpha = 0.95$.

The voltage drop across $2\text{k}\Omega$ resistance which is connected in the collector is 2V . Find the base current.

Solution:

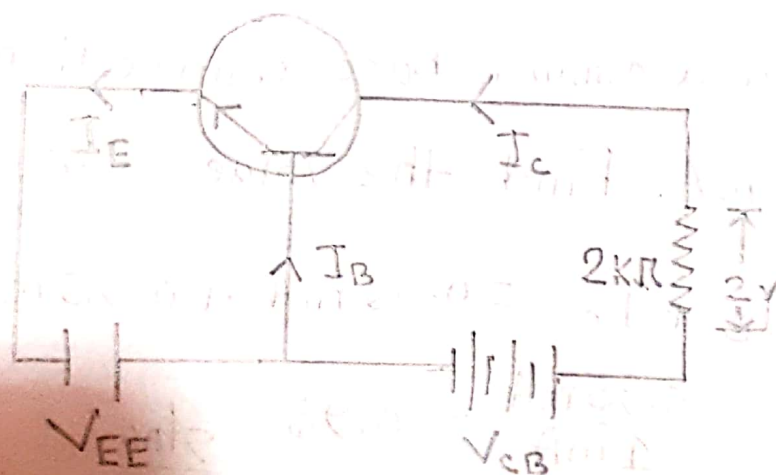

The voltage drop across R_C ($2k\Omega$) is $2V$

$$\therefore I_C = \frac{2V}{2k\Omega} = 1mA$$

$$\alpha = \frac{I_C}{I_E} \text{ or } I_E = \frac{I_C}{\alpha} = \frac{1mA}{0.95} = 1.05mA$$


Now,

$$I_E = I_B + I_C \text{ or } I_B = I_E - I_C = (1.05 - 1)mA$$

$$\therefore I_E = 0.05mA$$

Ans:

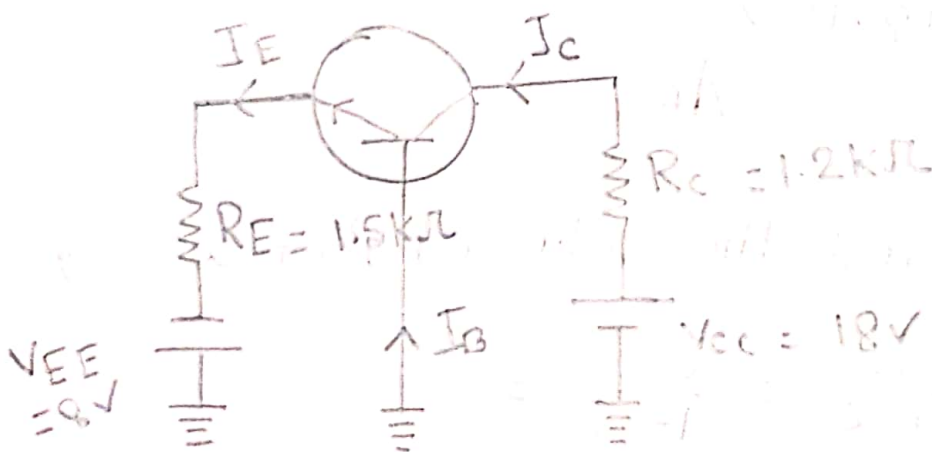Example 8.7: Determine I_C and V_{CB} . Assume the transistor to be of silicon.



Solution: Since the transistor is of silicon $V_{BE} = 0.7V$

Applying Kirchhoff's voltage law to the emitter-side loop, we get;

$$V_{EE} = I_E R_E + V_{BE}$$

$$\text{or, } I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

$$= \frac{8V - 0.7V}{1.5k\Omega} = 4.87 \text{ mA}$$

$$\therefore I_C \cong I_E = 4.87 \text{ mA}$$

Applying KVL to the collector-side loop, we have,

$$V_{CC} = I_C R_C + V_{CB}$$

$$\text{or, } V_{CB} = V_{CC} - I_C R_C$$

$$= 18V - 4.87 \text{ mA} \times 1.2k\Omega$$

$$\therefore V_{CB} = 12.16V$$

Ans:

Example 8.8: - Find the value of β if $\alpha = 0.9$

Solution: $\beta = \frac{\alpha}{1-\alpha} = \frac{0.9}{1-0.9} = 9$

Example 8.9: Calculate I_E in a transistor for which $\beta = 50$ and $I_B = 20\mu A$.


Solution: Here, $\beta = 50$, $I_B = 20 \mu A = 0.02 \text{ mA}$

$$\beta = \frac{I_C}{I_B} \text{ or, } I_C = \beta I_B = 50 \times 0.02 = 1 \text{ mA}$$

$$I_E = I_B + I_C = 0.02 + 1 = 1.02 \text{ mA}$$

Ans:

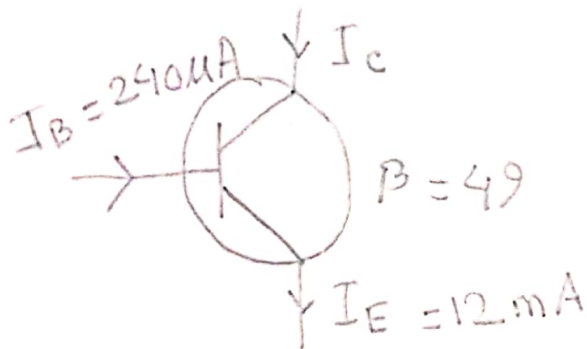Example 8.10: Find α and I_C (using α and β)



Solution:

$$\alpha = \frac{\beta}{1 + \beta} = \frac{49}{1 + 49} = 0.98$$

$$I_C = \alpha I_E = 0.98 \times (12 \text{ mA}) = 11.76 \text{ mA}$$


Also,

$$I_C = \beta I_B = 49 (240 \mu A) = 11.76 \text{ mA}$$

Ans:

Example 8.11: For a transistor $\beta = 45$ and voltage drop across $1\text{k}\Omega$ which is connected in the collector circuit is 1V . Find the base current for common emitter connection.

Solution:

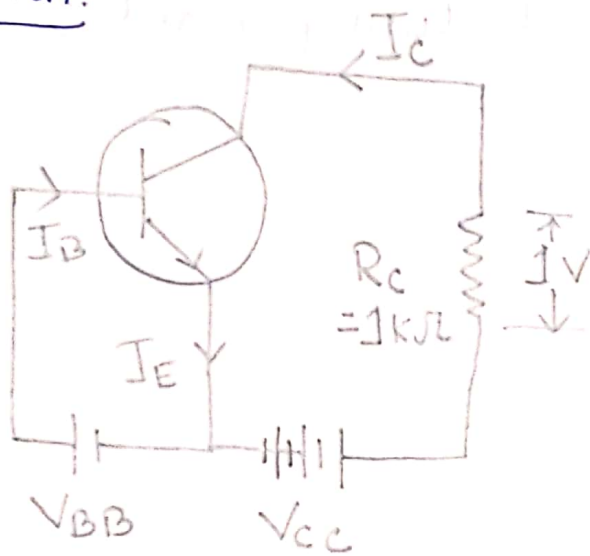

$$I_C = \frac{1\text{V}}{1\text{k}\Omega} = 1\text{mA}$$

Now,


$$\beta = \frac{I_C}{I_B} \text{ or } I_B = \frac{I_C}{\beta} = \frac{1}{45} = 0.022\text{mA}$$

Ans:

Example 8.12: A transistor is connected in common emitter configuration in which collector supply is 8V and the voltage drop across R_C connected in the collector circuit is 0.5V. The value of $R_C = 800\Omega$. If $\alpha = 0.96$ find:

- (i) collector emitter voltage
- (ii) base current.

Solution:

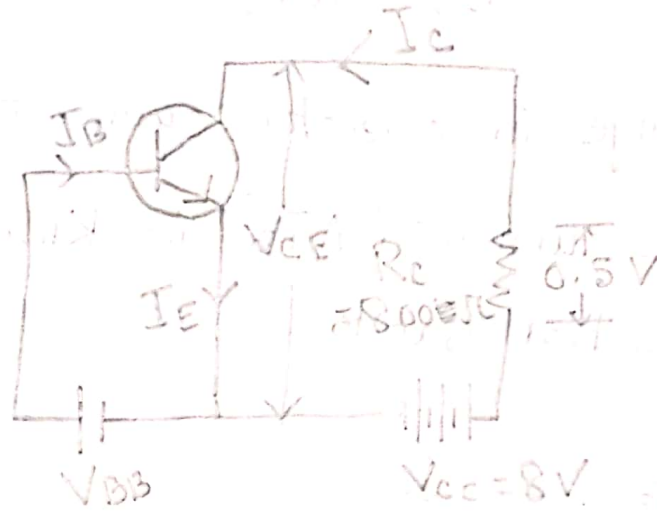

- (i) Collector emitter voltage,

$$V_{CE} = V_{CC} - 0.5 = 8 - 0.5 = 7.5V$$

- (ii) The voltage drop across R_C is 0.5V

$$\therefore I_C = \frac{0.5V}{800\Omega} = 0.625mA$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.96}{1-0.96} = 24$$

$$I_B = \frac{I_C}{\beta} = \frac{0.625}{24} = 0.026mA$$

Ans: