

International Islamic University Chittagong (IIUC)  
Department of Electronic and Telecommunication Engineering  
Semester End Examination

Program: **B.sc (Engg.)**  
Course Code: **EEE-1121**  
Total Marks: **50**

Semester: **Autumn 2023**  
Course Title: **Electrical Circuit I DC**  
Time: **2 Hours 30 Minutes**

- (i) Answer all the questions. The figures in the right-hand margin indicate full marks.  
(ii) Course Outcomes (COs) and Bloom's Levels are mentioned in additional Columns.

**Course Outcomes (COs) of the Questions**

<b>CLO1</b>	Understand the concepts of basic Circuit element, basic circuit, and basic circuit Laws and magnetic circuit laws.
<b>CLO2</b>	Analyze Electric Circuits and Components using suitable engineering analytical techniques.

**Bloom's Levels of the Questions**

Letter Symbols	R	U	Ap	An	E	C
Meaning	Remember	Understand	Apply	Analyze	Evaluate	Create

**PART A**

- Q1. a)** Obtain the node voltages in the circuit of Fig. 1

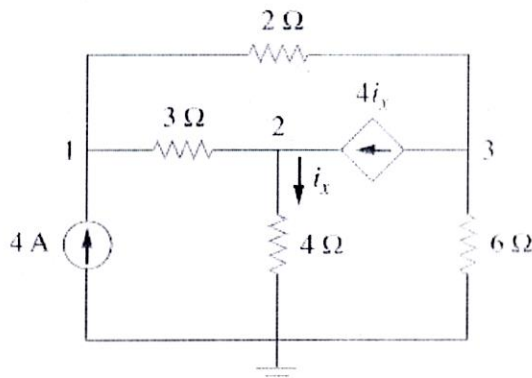


Fig. 1

**CLO2 Ap 5**

**OR**

- a)** Use Nodal Analysis to determine  $I_o$  in Fig. 2

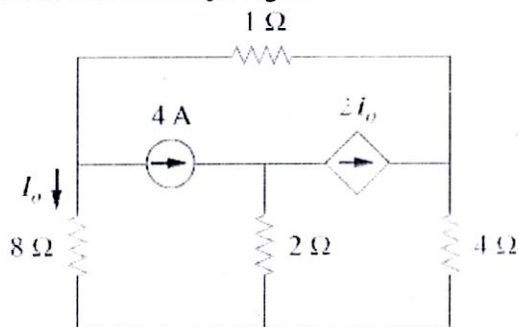


Fig. 2

**CLO2 Ap 5**

- b)** Use Mesh Analysis to determine  $I_o$  in the circuit of Fig. 3

**CLO2 Ap 5**

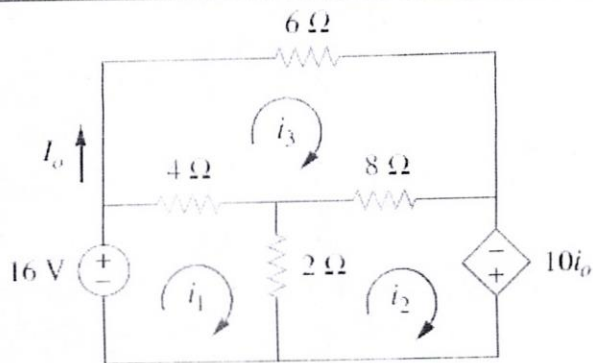


Fig. 3

OR

- b) Determine  $v_o$  and  $i_o$  in the circuit of Fig. 4 using mesh analysis.

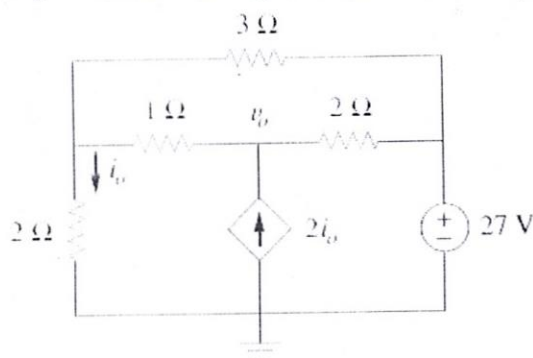


Fig. 4

CLO2

Ap

5

- Q2 a) Use Superposition to determine  $i$  in the circuit of Fig. 5

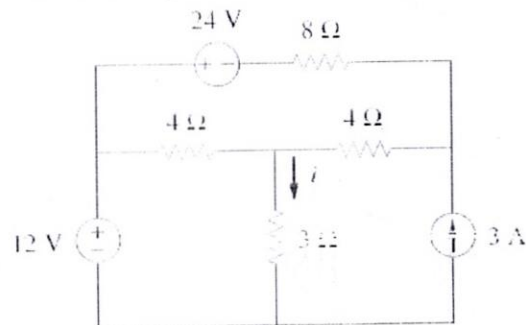


Fig.5

CLO2

Ap

5

- b) Determine the Thevenin Equivalent Circuit of the Circuit shown in Fig. 6 to the left of the terminal a-b. Then Find the current through  $R_L = 6\Omega$  and  $R_L = 36\Omega$ .

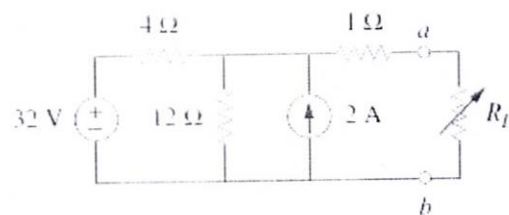


Fig. 6

CLO2

Ap

5

PART B

Q3.	a)	Explain the Statement: "Inductor acts like a short circuit to DC"	CLO1	U	3
	b)	Determine the equivalent inductance of the inductive network in Fig. 7	CLO2	Ap	3

Fig. 7

| **OR** |  |  |  |  |  |
|  | b) | Determine the equivalent capacitance of the circuit in Fig. 8 | CLO2 | Ap | 3 |

Fig. 8

|  | c) | In the Circuit of Fig. 9, Determine  $v_C$ ,  $i_L$ , energy stored in capacitor and inductor under DC condition. | CLO2 | Ap | 4 |

Fig. 9

| Q4. | a) | The switch in the circuit of Fig. 10 is closed for a long time. At  $t = 0$  the switch is opened. Calculate  $v(t)$  for  $t > 0$ . | CLO2 | Ap | 5 |

Fig. 10

|  | b) | The switch in Fig. 11 has been closed for a long time. At  $t = 0$ , the switch is opened. Determine  $i(t)$  for  $t > 0$ . | CLO2 | Ap | 5 |



Fig. 11

OR

- b) At  $t = 0$ , switch 1 in Fig. 12 is closed and switch 2 is closed 4s later. Determine  $i(t)$  for  $t > 0$ . Calculate  $i$  for  $t = 2$ s and  $t = 5$ s.

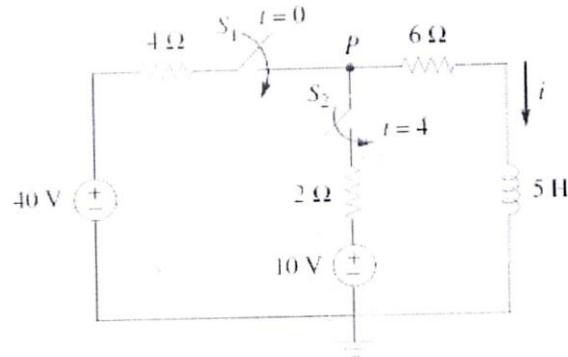


Fig. 12

CLO2

Ap

5

Q5.

a)

Define:

- Magnetic Flux Density
- Magnetizing Force

CLO1

U

3

b)

For the series magnetic circuit of Fig 13, Find the value of  $I$  required to develop a magnetic flux of  $4 \times 10^{-4}$  Wb.

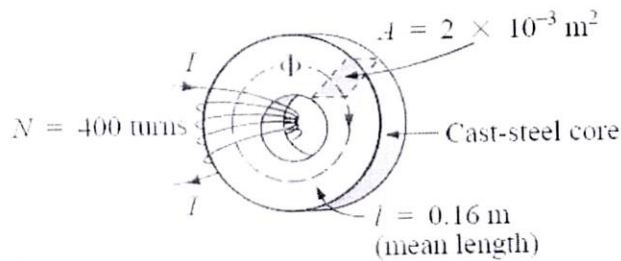


Fig. 13

CLO2

Ap

3

c)

For the electromagnet of Fig. 14, Determine the current  $I$  required to establish the indicated flux in the core.

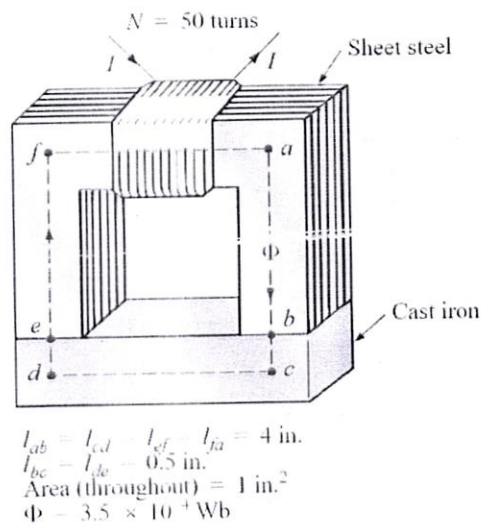


Fig. 14

CLO2

Ap

4

### APPENDIX

#### B-H Curve of 3 Materials

