

EEE-2421

MID  
Note?!

# Transformer

By -  
Jorowan Mahabub  
C201032  
Cell: 01521564257

→ Transformer is an electrical device that changes the magnitude of alternating voltage or current from one value to another.


→ It has no moving parts, so it is a static device

→ Same power level

→ Change voltage / current level

→ have 3 parts

Cone, Primary and Secondary

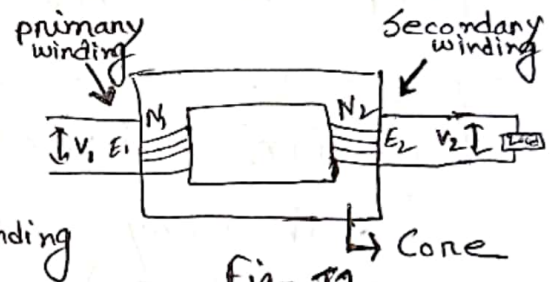

## Losses in [practical] Transformer:

① Copper Loss: The resistive heating losses in the primary and secondary windings of transformer is called copper loss.

→ This loss is proportional to the square of the current in the windings.

→ Total copper losses  $\Rightarrow I_1^2 R_1 + I_2^2 R_2$

→ Short Circuit Test is performed to determine the copper loss.

② Iron / Core Loss: The power losses that take place in its iron core are known as the Iron losses.

→ These losses occur due to alternating flux set up in the core.

→ Open Circuit Test is performed to determine.

→ 2 types of Iron loss are -

Eddy Current Losses, Hysteresis Losses

(a)

(b)

③ Leakage Flux: The flux which escape the core and pass through only one of the transformer windings are leakage fluxes

Eddy Current Losses: Because of time variation of flux in the magnetic material, Current is induced in the magnetic material is called Eddy Current.  
→ They are proportional to the square of the voltage applied to the transformer.

Hysteresis Losses: It occurs due to magnetization saturation in the core of the transformer.  
→ The eddy current and hysteresis loss both occurs in the core of the transformer

We can't Remove the hysteresis and eddy current losses. but we can reduce eddy current losses making the core by stacking thin sheets together. and reduce the hysteresis loss that the less area of the h. loop.

### Working Principle of Transformer:

Transformer works on the principle of Faradays Electromagnetic Mutual Induction between two coils which are magnetic coupled.

Fig-11 (Previous page)

by -  
Sonowon Mahabub  
C202032

According to the principle of mutual inductance, when an alternating voltage is applied to the primary winding of the transformer, an alternating flux  $\phi_m$  which is called as the mutual flux is produced in the core. This alternating flux links both the winding magnetically and induces EMF,  $E_1$  in the primary winding and



$E_2$  in the secondary winding of the transformer according to Faraday's Law of electromagnetic induction. The EMF ( $E_1$ ) is called as primary EMF and the EMF ( $E_2$ ) is known as Secondary EMF and being given as -

$$E_1 = -N_1 \frac{d\phi_m}{dt} \quad \text{and} \quad E_2 = -N_2 \frac{d\phi_m}{dt}$$

Therefore,  $\frac{E_2}{E_1} = \frac{N_2}{N_1}$

By -  
Jorowon  
Mahabub  
C201032  
Cell: 01521564157

From the given expression, it can be seen that the magnitude of EMFs  $E_1$  and  $E_2$  depend upon the number of turns in the primary and secondary winding of the transformers respectively, i.e., if  $N_2 > N_1$ , then  $E_2 > E_1$ , thus the transformer will be step-up and if  $N_2 < N_1$ , then  $E_2 < E_1$ , thus the transformer will be a step-down transformer.

If a load is <sup>now</sup> connected to across the secondary winding, the EMF  $E_2$  will cause a load current  $I_2$  to flow through the load. Therefore the transformer enables the transfer of power from one electric circuit to another electric circuit with a change in voltage level.

⇒ Construction:

where,


$V_P$  = is the primary voltage

$V_S$  =

$N_P$  = is the number of P. windings

$N_S$  =

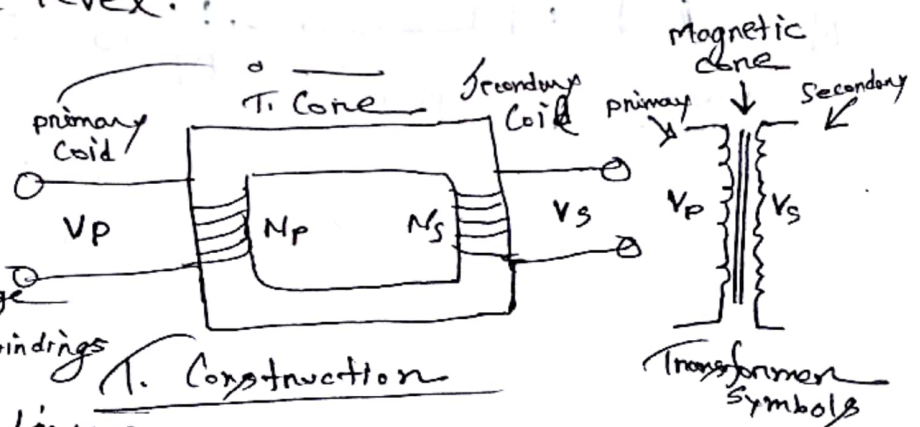$\phi(\text{Phi})$  = is the flux in linkage



## Transformer Rating in VA, But Why?



Ans: We know, the copper loss depends on Current and Core loss depends on voltage. And also we do not know the value or nature of load, so, we do not know the power factor. Thus, transformer rated in VA, KVA, MVA instead of KW, MW.

$$\text{Turn Ratio} = K = \frac{E_2}{E_1} = \frac{N_2}{N_1}$$
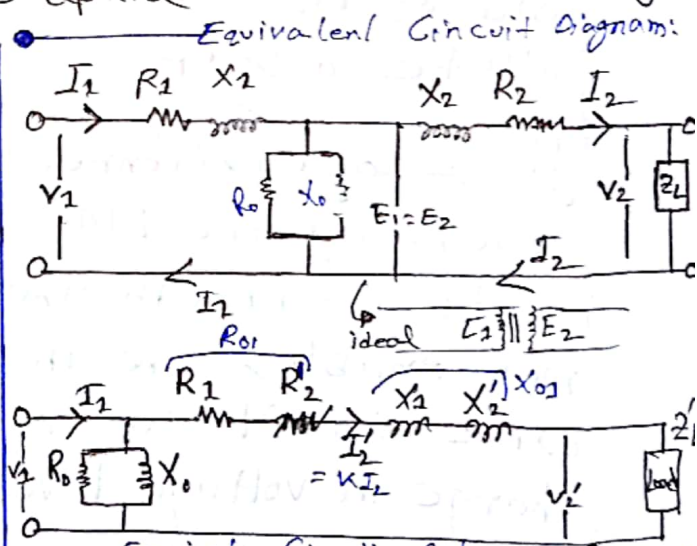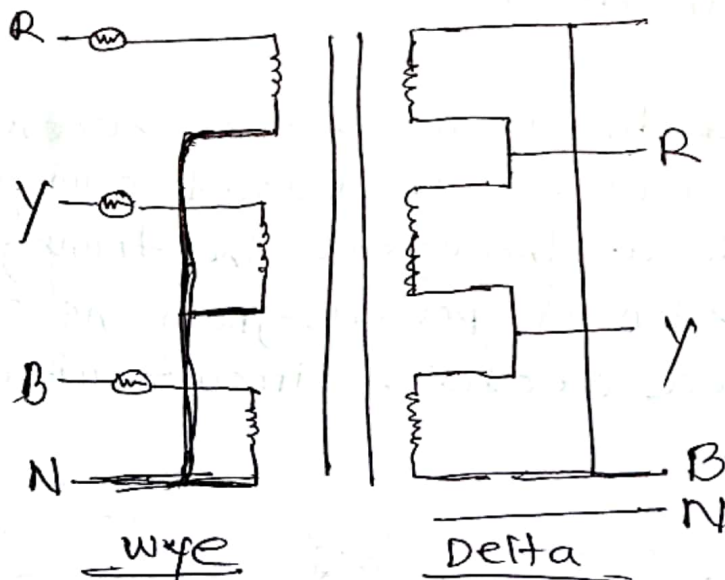
## Transformer Do not Operate in DC, Why?

Ans: As we need alternating flux for generating electromotive force at both winding for that reason we need alternating current which is come from A.C source but in DC source, we can't have alternate of current so it can't generate alternate flux and transformer can't have emf. That's why on DC, transformer doesn't operate.  
 ⇒ see different kind of Transformer types from my source.

Single Phase: Single phase power is a ~~two~~ <sup>two</sup>-wire ac power circuit. Three phase: Three phase power is a three-wire ac (alternating current) with each phase ac signal 120 electrical degrees apart.



Equivalent Circuit - Referred to Primary

$$\begin{aligned} Z_{01} &= R_{01} + jX_{01} \quad (\text{Total impedance}) \\ R_{01} &= R_1 + R_2' & Z_{02} &= R_{02} + jX_{02} \\ X_{01} &= X_1 + X_2' & R_{02} &= R_2 + R_1' \\ & & X_{02} &= X_2 + X_1' \end{aligned}$$


by - Sonowar Mahabub  
 C201032  
 Cell: 02521564157


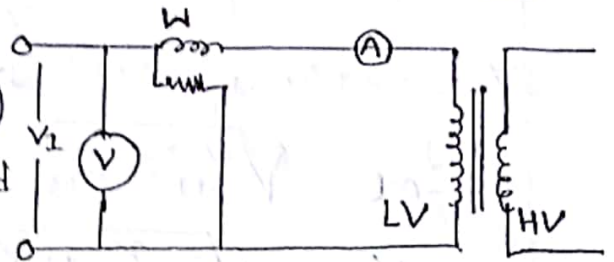
## \* Open Circuit Test :


open circuit test or no load test is performed to determine Core losses of the transformer.

Usually High Voltage (HV) winding is kept open and the low voltage (LV) winding is connected to its normal supply.



A Wattmeter (W), ammeter (A) and voltmeter (V) are connected to the LV winding as shown in the figure. Now applied voltage is slowly increased from zero to Normal rated value of the LV side with the help of a variac.

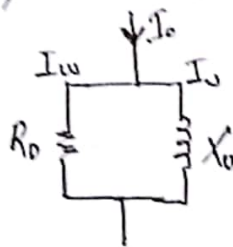- The wattmeter measures the iron losses of the transformer
- The ammeter measures the no load current,  $I_0$  (is very small)
- The voltmeter measures the applied voltage in the LV winding



$$W = V_1 I_0 \cos \phi_0$$

$$\text{power factor, P.F., } \cos \phi = \frac{W}{V_0 I_0}$$

$$X_0 = \frac{V_1}{I_v}, R_0 = \frac{V_1}{I_w}, Z_0 = \sqrt{R_0^2 + X_0^2}$$

Core losses

$$I_w = I_0 \cos \phi_0$$

$$I_v = I_0 \sin \phi_0$$

Where,

$W$  = Wattmeter Reading |  $I_w$  = Core-loss Component of no-load Current

$V_1$  = Applied Voltage

$I_0$  = Ammeter Reading

$I_v$  = Magnetizing " " " "

## Short Circuit Test :

Short circuit test or impedance test is performed to determine  $R_{01}$  (or,  $R_{02}$ ),  $X_{01}$  (or,  $X_{02}$ ) and full load copper losses of the transformer. The LV side of transformer is short circuited and wattmeter (W), voltmeter (V) and ammeter (A) are connected on the HV side of the transformer. Voltage is applied to the HV side and increased from the zero until the ammeter reading equals rated current. All the readings are taken at this rated current.

$$W_s = P_c = I_1^2 R_1 + I_2^2 R_2' = I_1^2 R_{01}$$


$$R_{01} = \frac{W_s}{I_1^2} \quad \text{--- (1)}$$

$$V_{sc} = I_1 \times Z_{01} \Rightarrow Z_{01} = \frac{V_{sc}}{I_1} \quad \text{--- (2)}$$

$$Z_{01} = \sqrt{X_{01}^2 + R_{01}^2}$$

or,  $X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$  (using (1) and (2))

Short Circuit P.F. =  $\cos \phi_2 = \frac{W_s}{V_{sc} \times I_1}$  |  $V_{sc}$  = Applied Voltage  
 $I_1$  = Ammeter reading

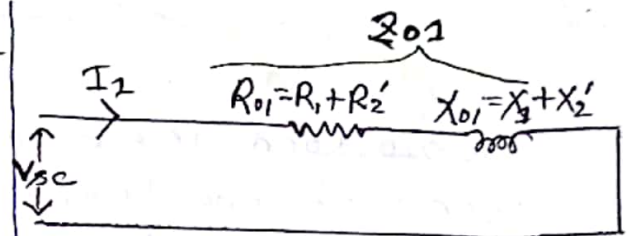

$W_s$  = wattmeter reading  
 = full load copper loss ( $P_c$ )

## Transformer's Math Eeqn

### (01) EMF eqn of Transformer:

$$E_1 = -N_1 \frac{d\phi}{dt}$$

$$E_2 = -N_2 \frac{d\phi}{dt}$$

$E_1/E_2 \rightarrow$  EMF of primary winding  
 $N_1/N_2 \rightarrow$  Number of turns in primary  
 $\phi \rightarrow$  Maximum Flux

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

### (02) Turns Ratio:

Turns ratio,  $a = \frac{N_1}{N_2}$

Transformer Ratio,  $K = \frac{N_2}{N_1} = \frac{E_2}{E_1}$

$\therefore a = \frac{1}{K}$   
 $K = \frac{1}{a}$

### (03) Voltage Regulation:

$$= \frac{V_{no-load} - V_{on-load}}{V_{no-load}} \times 100$$

(04)  $\Rightarrow \frac{V_{No-load} - V_{on-load}}{V_{no-load}} \times 100$

$V_{no-load}$  = No-Load Secondary Voltage

$V_2$  = Secondary Voltage on load

by  
 Jono war Mahabub  
 6201032

Cell: 01521564157



# Motor Sizing

Motor: Converts electrical energy into mechanical energy. Conversion factor: 1HP = 746 Watts


Speed (N): The number of revolutions per minute of the motor.  $n = \frac{N}{60}$  revs per second  $\omega = 2\pi N/60$  radians per second

Torque: The force with which a motor turns is called Torque. measured in Nm.

Relation bet<sup>n</sup> Power, Speed, Torque:  $P = \frac{2\pi \times T \times N}{60}$

$$\text{RMS power} = \sqrt{\frac{P_1^2 t_1 + P_2^2 t_2 + P_3^2 t_3 + \dots + P_n^2 t_n}{t_1 + t_2 + t_3 + \dots + t_n}}$$

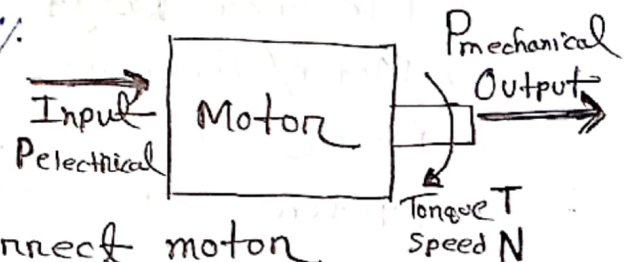Efficiency:  $\eta = \frac{\text{output}}{\text{input}} \times 100\%$



⇒ Motor sizing refers to the process of picking the correct motor for a given load.

→ For load torque is constant then choosing a motor whose rated torque is slightly above the torque required by the load. The load ~~st~~ torque should be bet<sup>n</sup> 75% - 100% for the rated motor torque with 95% being an ideal choice.

⇒ Motor Torque > Load Torque, the Load will Accelerate  
Accelerating Torque =  $T_{\text{motor}} - T_{\text{load}}$

→ Just go through the pdf named "Motor Duty" and Read ☺

by -

Sonowon Mahabub

C201032

Cell: 02521564157

## DC Machines

by -  
Sonowon Mahabub  
C201032  
Cell: 02521564157

⇒ DC machines DC outputs just because they have a mechanism converting AC voltages to DC voltages. - This converting mechanism is called commutation.

→ DC machines are also called Commutating Machines.

Magnetic Field: the portion of space near a magnetic body or a current carrying body in which the magnetic forces due to the body or current can be detected.

\* Fleming Right Hand Rule for → Generator

\* Fleming **Left** Hand Rule for → Motor

→ Motor/Generator have 2 parts are -

(a) Rotor (যা ঘুরতে থাকবে।)

(b) Stator (যা স্থির থাকবে।)

↪ creates flux

→ Both DC and AC Generator convert mechanical power to electrical power. Both of these produce electrical power based on the principle of Faraday's law of electromagnetic induction.

Faraday's 1st Law Whenever a conductor is rotated in magnetic field emf is induced in it. If the conductor is closed, current will flow through it which is known as induced current.

The induced emf in a coil is equal to the rate of change of flux linkage.

$$E = -N \frac{d\phi}{dt}$$

Faraday's 2nd Law

Right Hand Rule: Thumb (সুপার) → indicates Motion

→ Index finger indicates → the Magnetic field

→ Middle finger indicates the direction of Current.

Left Hand Rule: F → Force, B → Flux Density, I → Current