

# International Islamic University Chittagong (IIUC)


## Department of Electronic and Telecommunication Engineering




### Final Examination

Program: **B.sc (Engg.)**  
 Course Code: **ETE-1121**  
 Total Marks: **50**

Semester: **Autumn 2022**  
 Course Title: **Electrical Circuit I DC**  
 Time: **2 Hours 30 Minutes**

(i) Answer all the questions. The figures in the right-hand margin indicate full marks.						
(ii) Course Outcomes (COs) and Bloom's Levels are mentioned in additional Columns.						
Course Outcomes (COs) of the Questions						
CLO 1	Understand the concepts of basic Circuit element, basic circuit, and basic circuit Laws and magnetic circuit laws.					
CLO 2	Introduce series parallel circuit and different network theorem to analysis the circuits.					
Bloom's Levels of the Questions						
Letter Symbols	R	U	Ap	An	E	C
Meaning	Remember	Understand	Apply	Analyze	Evaluate	Create

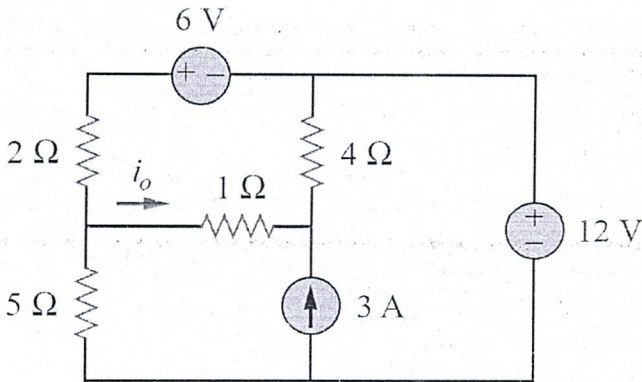PART A						
<b>Q1</b>	<b>a)</b>	"Nodal analysis, which is based on a systematic application of Kirchhoff's current law (KCL), and mesh analysis, which is based on a systematic application of Kirchhoff's voltage law (KVL)" Is above statement true? Justify the Statement. Also explain the terms " <b>super node</b> " and " <b>super Mesh</b> ".	<b>CLO2</b>	<b>E</b>	<b>5</b>	
	<b>b)</b>	Use <i>mesh analysis</i> to obtain $i_o$ in the circuit of <b>Fig. 1(b)</b> .  <div style="text-align: center;">  </div> <p style="text-align: center;"><b>Figure 1(b)</b></p>	<b>CLO2</b>	<b>Ap</b>	<b>5</b>	
<b>OR</b>						

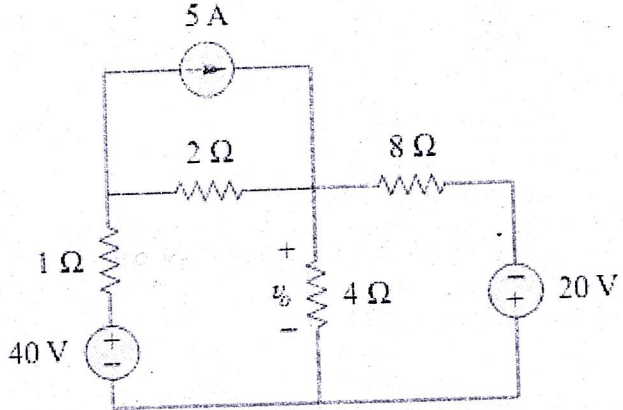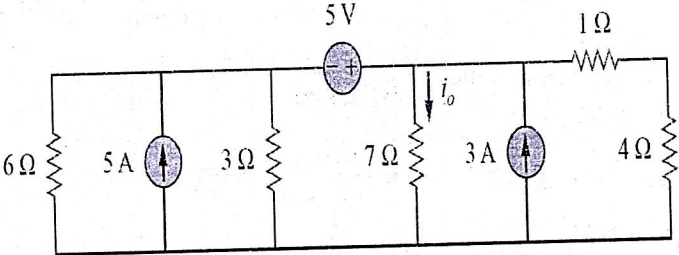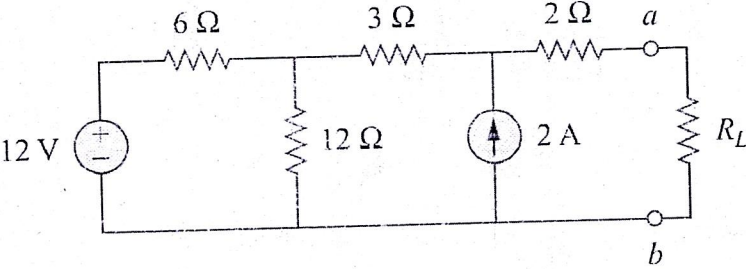	<p>Using <i>nodal analysis</i>, find <math>V_o</math> in the circuit of <b>Fig. 1(b)</b></p>  <p style="text-align: center;"><b>Figure 1(b)</b></p>	CLO2	Ap	5
Q2	<p>a) Find <math>i_o</math> in the circuit of <b>Fig. 2(a)</b> using <i>source transformation</i>.</p>  <p style="text-align: center;"><b>Figure 2(a)</b></p> <p>b) Find the value of <math>R_L</math> for <i>maximum power transfer</i> in the circuit of <b>Fig. 2(b)</b>. Find the <i>maximum power</i>.</p>  <p style="text-align: center;"><b>Figure 2(b)</b></p> <p style="text-align: center;"><b>OR</b></p>	CLO2	Ap	5



		Find the <b>Norton equivalent circuit</b> for the circuit in <b>Fig. 2(b)</b> , at terminals a-b.	CLO2	Ap	5
--	--	---	------	----	---

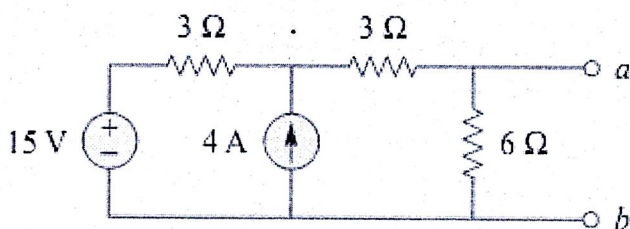


Figure 2 (b)

### PART B

Q3	a)	"The equivalent capacitance of series-connected capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances" Prove the statement.	CLO2	E	5
	b)	In <b>Fig. 3(b)</b> , let $v_C(0) = 15$ V. Find $v_C$ , $v_x$ , and $i_x$ for $t > 0$ .	CLO2	Ap	5

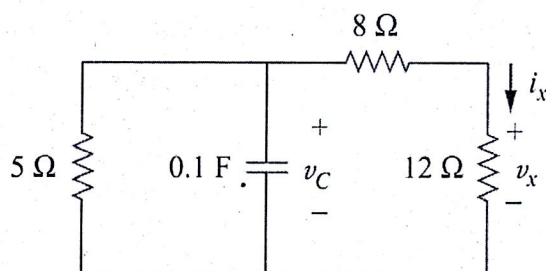


Figure 3(b)

OR

		Find $i(t)$ in the circuit of <b>Fig. 3(b)</b> for $t > 0$ . Assume that the switch has been closed for a long time.	CLO2	Ap	5
--	--	--	------	----	---


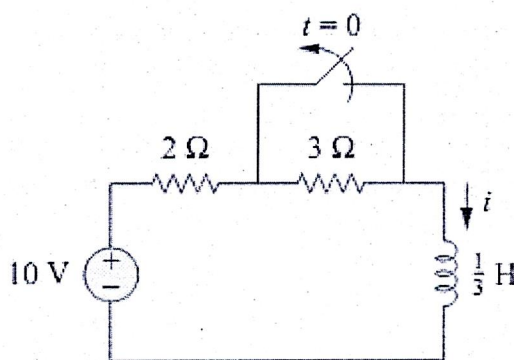
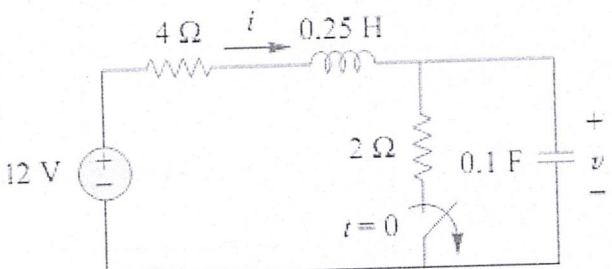
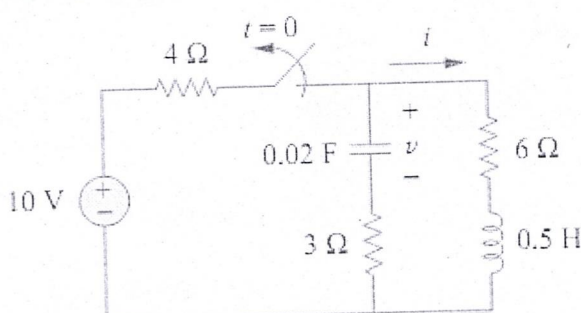


Figure 3(b)

Q4	a)	<p>The switch in <b>Fig. 4(a)</b> has been closed for a long time. It is open at <math>t=0</math>. Find: (i) <math>i(0^+)</math>, <math>v(0^+)</math> (ii) <math>di(0^+)/dt</math>, <math>dv(0^+)/dt</math> (c) <math>i(\infty)</math>, <math>v(\infty)</math>.</p>  <p style="text-align: center;">Figure 4(a)</p>	CLO2	Ap	5
	b)	<p>Find <math>i(t)</math> in the circuit of <b>Fig. 4(b)</b>. Assume that the circuit has reached steady state at <math>t = 0^-</math>.</p>  <p style="text-align: center;">Figure 4(b)</p>	CLO2	Ap	5
OR					
		<p>For the circuit in <b>Fig. 4(b)</b>, find <math>v(t)</math> and <math>i(t)</math> for <math>t &gt; 0</math>. Consider <math>R=4\Omega</math>.</p>  <p style="text-align: center;">Figure 4(b)</p>	CLO2	Ap	5
Q5	a)	<p>Explain the terms "<i>flux</i>" and "<i>magnetic force</i>." Also Briefly Explain <i>Ampère's Circuital Law</i> for magnetic circuits.</p>	CLO1	U	5

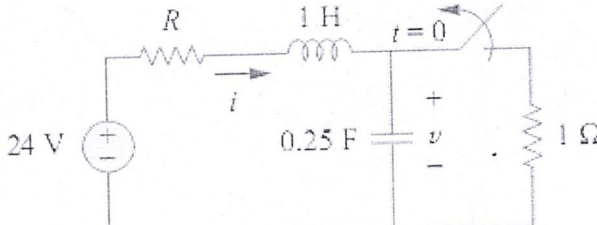

- b) Find the value of  $I$  required to establish a magnetic flux of  $\Phi = 0.75 \times 10^{-4} \text{ Wb}$  in the series magnetic circuit in Fig. 5(b).

CLO2

Ap

5

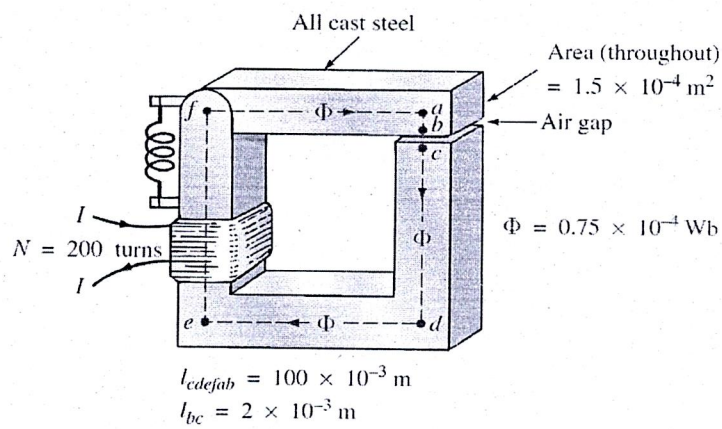


Figure 5(b)

### Appendix:

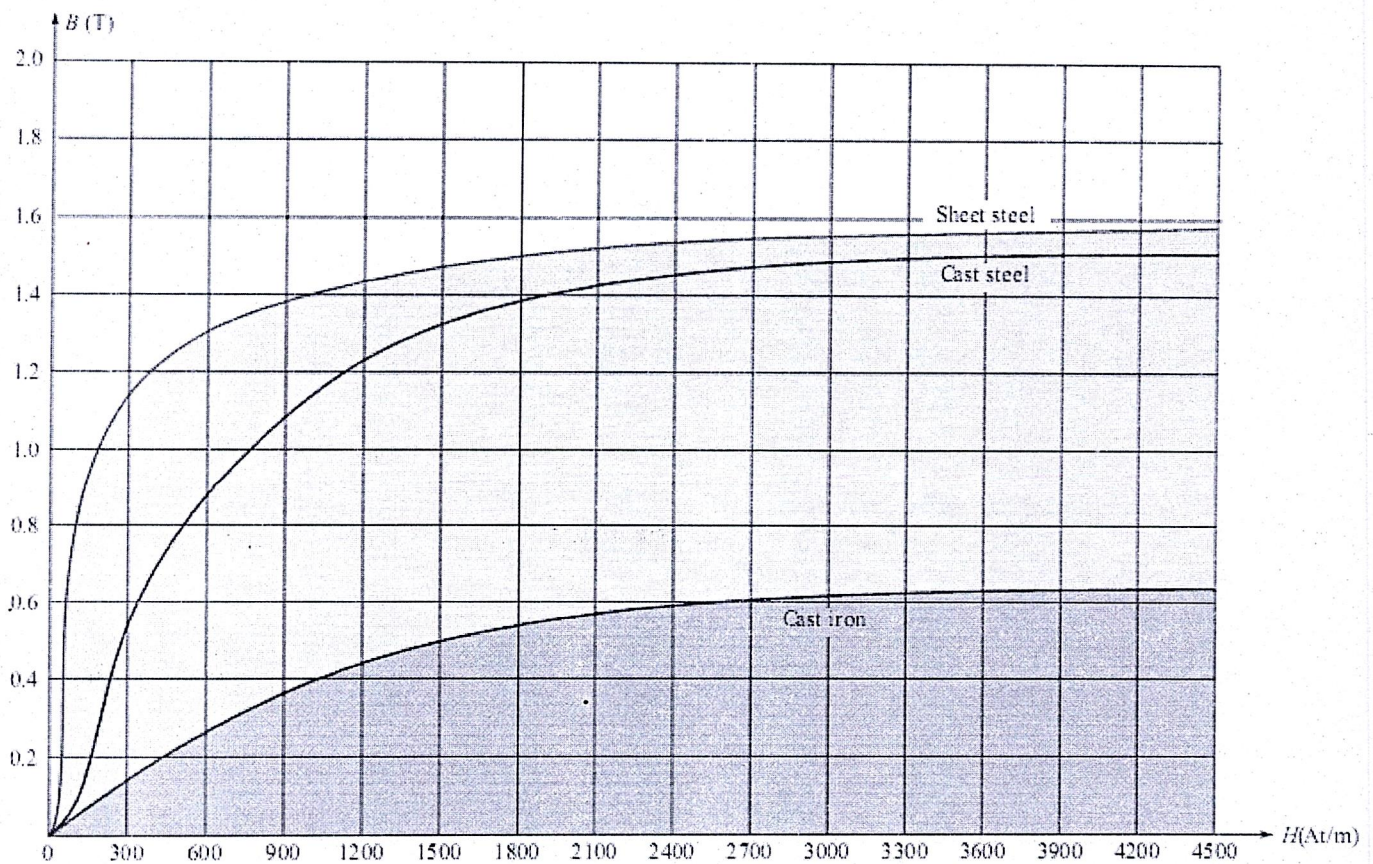


Figure Appendix 1